

Solutions to *The Art of Electronics 3rd Edition*

December 11, 2023

Contents

1	Solutions for Chapter 1	5	1.38 Exercise 1.38	28
1.1	Exercise 1.1	5	1.39 Exercise 1.39	28
1.2	Exercise 1.2	5	1.40 Exercise 1.40	28
1.3	Exercise 1.3	5	1.41 Exercise 1.41	29
1.4	Exercise 1.4	6	1.42 Exercise 1.42	30
1.5	Exercise 1.5	7	1.43 Exercise 1.43	30
1.6	Exercise 1.6	7	1.44 Exercise 1.44	30
1.7	Exercise 1.7	8		
1.8	Exercise 1.8	9	2	Solutions for Chapter 2
1.9	Exercise 1.9	10	2.1	Exercise 2.1
1.10	Exercise 1.10	12	2.2	Exercise 2.2
1.11	Exercise 1.11	14	2.3	Exercise 2.3
1.12	Exercise 1.12	15	2.4	Exercise 2.4
1.13	Exercise 1.13	15	2.5	Exercise 2.5
1.14	Exercise 1.14	16	2.6	Exercise 2.6
1.15	Exercise 1.15	16	2.7	Exercise 2.7
1.16	Exercise 1.16	17	2.8	Exercise 2.8
1.17	Exercise 1.17	17	2.9	Exercise 2.9
1.18	Exercise 1.18	18	2.10	Exercise 2.10
1.19	Exercise 1.19	18	2.11	Exercise 2.11
1.20	Exercise 1.20	18	2.12	Exercise 2.12
1.21	Exercise 1.21	18	2.13	Exercise 2.13
1.22	Exercise 1.22	19	2.14	Exercise 2.14
1.23	Exercise 1.23	19	2.15	Exercise 2.15
1.24	Exercise 1.24	20	2.16	Exercise 2.16
1.25	Exercise 1.25	21	2.17	Exercise 2.17
1.26	Exercise 1.26	21	2.18	Exercise 2.18
1.27	Exercise 1.27	22	2.19	Exercise 2.19
1.28	Exercise 1.28	23	2.20	Exercise 2.20
1.29	Exercise 1.29	23	2.21	Exercise 2.21
1.30	Exercise 1.30	24	2.22	Exercise 2.22
1.31	Exercise 1.31	24	2.23	Exercise 2.23
1.32	Exercise 1.32	24	2.24	Exercise 2.24
1.33	Exercise 1.33	25	2.25	Exercise 2.25
1.34	Exercise 1.34	25	2.26	Exercise 2.26
1.35	Exercise 1.35	25	2.27	Exercise 2.27
1.36	Exercise 1.36	26	2.28	Exercise 2.28
1.37	Exercise 1.37	26	2.29	Exercise 2.29
			2.30	Exercise 2.30

Solutions for Chapter 1

Exercise 1.1

(a) $R = 5 \text{ k}\Omega + 10 \text{ k}\Omega = \boxed{15 \text{ k}\Omega}$

(b) $R = \frac{R_1 R_2}{R_1 + R_2} = \frac{5 \text{ k}\Omega \times 10 \text{ k}\Omega}{5 \text{ k}\Omega + 10 \text{ k}\Omega} = \boxed{3.33 \text{ k}\Omega}$

Exercise 1.2

$$P = IV = \left(\frac{V}{R}\right) V = \frac{(12 \text{ V})^2}{1 \Omega} = \boxed{144 \text{ W}}$$

Exercise 1.3

Consider a simple series resistor circuit.

Figure 1.1: A basic series circuit.



By KVL and Ohm's law


$$V = V_1 + V_2 = R_1 \cdot I + R_2 \cdot I = (R_1 + R_2) \cdot I = R \cdot I$$

where

$$\boxed{R = R_1 + R_2}$$

is the resistance of R_1 and R_2 in series. Now, consider a simple parallel resistor circuit.

Figure 1.2: A basic parallel circuit.

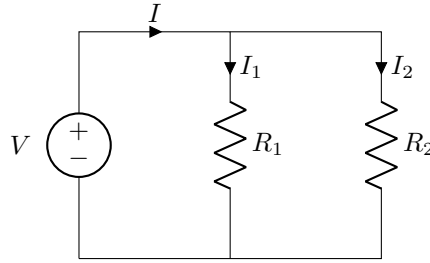

By KCL and Ohm's law

$$I = I_1 + I_2 = \frac{V}{R_1} + \frac{V}{R_2} = \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \cdot V$$

solving for V as a function of I we get

$$V = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} \cdot I = \frac{R_1 R_2}{R_1 + R_2} \cdot I = R \cdot I$$

where

$$R = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2}$$

is the resistance of R_1 and R_2 in parallel.

Exercise 1.4

We know that the resistance R_{12} ¹ of two resistors R_1 and R_2 in parallel is given by

$$R_{12} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

Now, the resistance R_{123} of three resistors R_1 , R_2 and R_3 in parallel is equal to the resistance of two resistors R_{12} (the resistance between R_1 and R_2 in parallel) and R_3 in parallel, then

$$R_{123} = \frac{1}{\frac{1}{R_{12}} + \frac{1}{R_3}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

We will prove by induction that the resistance $R_{1\dots n}$ of n resistances R_1, R_2, \dots, R_n in parallel is given by

$$R_{1\dots n} = \frac{1}{\sum_{i=1}^n \frac{1}{R_i}}$$

First, it's trivial to show that with $n = 1$ the equality holds. Now, we will assume that the equality is satisfied for $n = k$, that is

$$R_{1\dots k} = \frac{1}{\sum_{i=1}^k \frac{1}{R_i}}$$

¹Here we have only assigned a name to the resistance in parallel between R_1 and R_2 .

Then, we must show that equality holds for $n = k + 1$. Thus, the resistance $R_{1\dots(k+1)}$ of $(k + 1)$ resistances R_1, R_2, \dots, R_{k+1} in parallel is equal to the resistance of two resistors $R_{1\dots k}$ and R_{k+1} in parallel, then

$$R_{1\dots(k+1)} = \frac{1}{\frac{1}{R_{1\dots k}} + \frac{1}{R_{k+1}}} = \frac{1}{\sum_{i=1}^k \frac{1}{R_i} + \frac{1}{R_{k+1}}} = \frac{1}{\sum_{i=1}^{k+1} \frac{1}{R_i}}$$

where we have proved that equality holds for $n = k + 1$. Finally, the resistance of n resistors in parallel is given by

$$R_{1\dots n} = \frac{1}{\sum_{i=1}^n \frac{1}{R_i}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}}$$

Exercise 1.5

Given that $P = \frac{V^2}{R}$, we know that the maximum voltage we can achieve is 15 V and the smallest resistance we can have across the resistor in question is 1 k Ω . Therefore, the maximum amount of power dissipated can be given by

$$P = \frac{V^2}{R} = \frac{(15 \text{ V})^2}{1 \text{ k}\Omega} = \boxed{0.225 \text{ W}}$$

This is less than the 0.25 W power rating.

Exercise 1.6

- (a) The total current required by New York City that will flow through the cable is

$$I = \frac{P}{V} = \frac{1 \times 10^{10} \text{ W}}{115 \text{ V}} = 86.96 \text{ MA}$$

Therefore, the total power lost per foot of cable can be calculated by:

$$P = I^2 R = (86.96 \times 10^6 \text{ A})^2 \times (5 \times 10^{-8} \Omega/\text{ft}) = \boxed{3.78 \times 10^8 \text{ W/ft}}$$

- (b) The length of cable over which all $1 \times 10^{10} \text{ W}$ will be lost is:

$$L = \frac{1 \times 10^{10} \text{ W}}{3.78 \times 10^8 \text{ W/ft}} = \boxed{26.45 \text{ ft}}$$

- (c) To calculate the heat dissipated by the cable, we can use the Stefan-Boltzmann equation $T = \sqrt[4]{\frac{P}{A\sigma}}$, with A corresponding to the cylindrical surface area of the 26.45 ft section of 1-foot diameter cable. Note that σ is given in cm^2 , so we will need to use consistent units.

$$A = \pi DL = \pi \times 30.48 \text{ cm} \times 806.196 \text{ cm} = 7.72 \times 10^4 \text{ cm}^2$$

Therefore,

$$T = \sqrt[4]{\frac{P}{A\sigma}} = \sqrt[4]{\frac{1 \times 10^{10} \text{ W}}{7.72 \times 10^4 \text{ cm}^2 \times 6 \times 10^{-12} \text{ W/K}^4/\text{cm}^2}} = \boxed{12,121 \text{ K}}$$


This is indeed a preposterous temperature, more than twice that at the surface of the Sun! The solution to this problem is that power should be transmitted along long distances at high voltage. This greatly reduces $I^2 R$ losses. For example, a typical high voltage line voltage is 115 kV. At this voltage, the power loss per foot of cable is only 378 W per foot. Intuitively, we know that reducing current allows for lower power dissipation. We can deliver the same amount of power with a lower current by using a higher voltage.

Exercise 1.7

A $20,000\ \Omega\ \text{V}^{-1}$ meter read, on its 1 V scale, puts a $20,000\ \Omega\ \text{V}^{-1} \cdot 1\ \text{V} = 20,000\ \Omega = 20\ \text{k}\Omega$ resistor in series with an ideal ammeter (ampere meter). Also, a voltage source with an internal resistance is equivalent to an ideal voltage source with its internal resistance in series.

(a) In the first question, we have the following circuit:

Figure 1.3: A voltage source with internal resistance and a $20,000\ \Omega\ \text{V}^{-1}$ meter read in its 1 V scale.

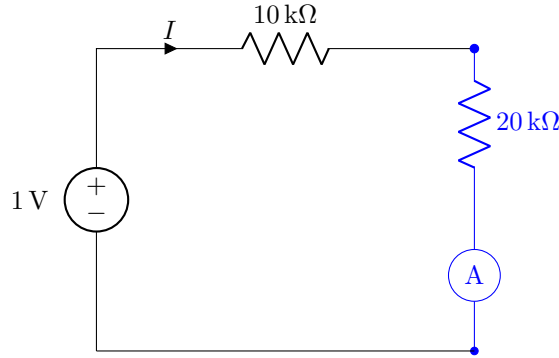


Then, we have that the current in the ideal ammeter and the voltage in the meter resistance are given by²

$$I = \frac{1\ \text{V}}{10\ \text{k}\Omega + 20\ \text{k}\Omega} = \boxed{0.0333\ \text{mA}} \quad \text{and} \quad V = 0.0333\ \text{mA} \times 20\ \text{k}\Omega = \boxed{0.666\ \text{V}}$$

(b) In the second question, we have the following circuit:

Figure 1.4: A $10\ \text{k}\Omega - 10\ \text{k}\Omega$ voltage divider and a $20,000\ \Omega\ \text{V}^{-1}$ meter read in its 1 V scale.

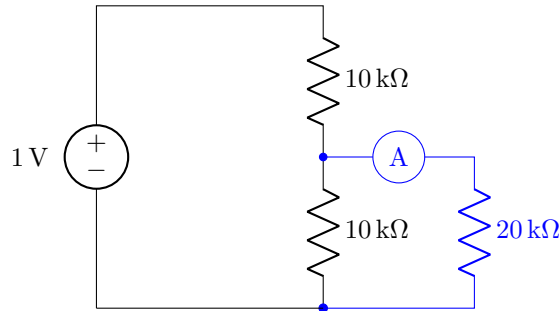

Now, we can obtain the Thévenin equivalent circuit of circuit in Figure 1.4 with

$$R_{\text{Th}} = \frac{10\ \text{k}\Omega \cdot 10\ \text{k}\Omega}{10\ \text{k}\Omega + 10\ \text{k}\Omega} = 5\ \text{k}\Omega$$


²When a meter only measures currents, it puts a resistance in series to measure the current through that resistance and internally converts that current into voltage to *measure voltages*.

and

$$V_{Th} = 1 \text{ V} \cdot \frac{10 \text{ k}\Omega}{10 \text{ k}\Omega + 10 \text{ k}\Omega} = 0.5 \text{ V}$$

Then, we have the following equivalent circuit:

Figure 1.5: Thévenin equivalent circuit of circuit in Figure 1.4.

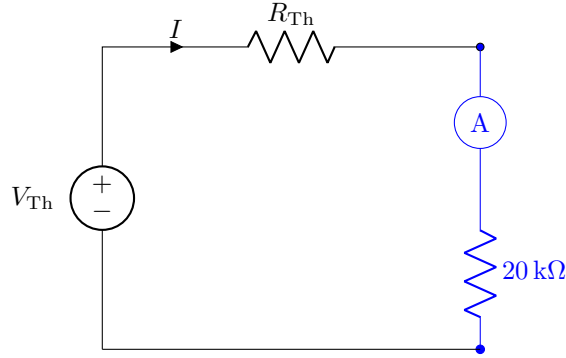


Finally, we have that the current in the ideal ammeter and the voltage in the meter resistance are given by

$$I = \frac{0.5 \text{ V}}{5 \text{ k}\Omega + 20 \text{ k}\Omega} = \boxed{0.02 \text{ mA}} \quad \text{and} \quad V = 0.02 \text{ mA} \cdot 20 \text{ k}\Omega = \boxed{0.4 \text{ V}}$$

Exercise 1.8

(a) In the first part, we have the following circuit:

Figure 1.6: 50 μA ammeter with 5 $\text{k}\Omega$ internal resistance (shown in blue) in parallel with shunt resistor.

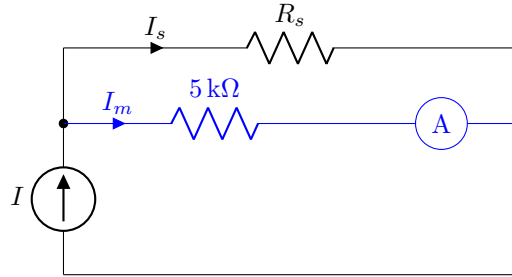

We want to measure I for 0-1 A, and the ideal ammeter measures up to 50 μA . To find what shunt resistance R_s allows us to do so, we set $I = 1 \text{ A}$ and $I_m = 50 \mu\text{A}$. By KCL we know $I_s = 0.999950 \text{ A}$. To determine R_s , we still need to find the voltage across it. We can find this voltage by doing


$$V = I_m R_m = 50 \mu\text{A} \cdot 5 \text{ k}\Omega = 0.25 \text{ V}$$

Then we simply do

$$R_s = \frac{V}{I_s} = \frac{0.25 \text{ V}}{0.999950 \text{ A}} = \boxed{0.25 \Omega}$$

(b) In the second part, we have the following circuit:

Figure 1.7: 50 μA ammeter with 5 $\text{k}\Omega$ internal resistance (shown in blue) with a series resistor.

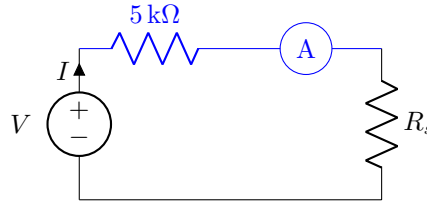

We want to measure V for 0-10 V, and the ideal ammeter measures up to 50 μA . To find the series resistance R_s , we set $V = 10 \text{ V}$ and $I = 50 \mu\text{A}$. Then we solve


$$\frac{V}{I} = 5 \text{ k}\Omega + R_s$$

$$R_s = \frac{10 \text{ V}}{50 \mu\text{A}} - 5 \text{ k}\Omega = \boxed{195 \text{ k}\Omega}$$

Exercise 1.9


In order to measure resistance well above the range of your multimeter, you need to get creative. We will be using the multimeter in voltmeter mode. Lets start by connecting our DC voltage source, voltmeter, and the high-value resistor in series. (The reason for doing this will become clear later).

Figure 1.8: Connection of three components.

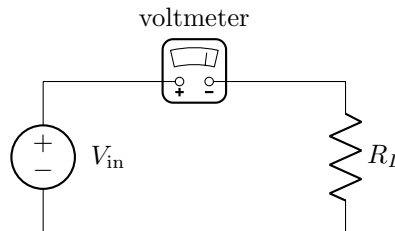

V_{in} is our test voltage, and R_L is our leakage resistance. We need to revise the model for our voltmeter.


Figure 1.9: The voltmeter is now modeled as a resistor with value R_M .

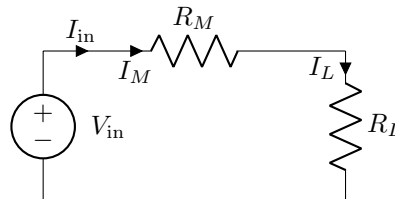

The current flowing through our meter (modeled by the resistor R_M) is equal to the current flowing through the leakage resistor. This is also equal to the current supplied from our voltage source.

$$I_M = I_L = I_{in}$$

Figure 1.10: Voltage and current labels are added.

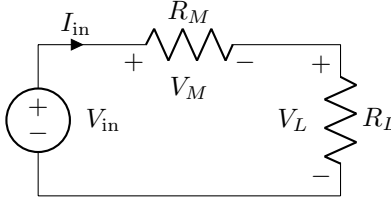

Notice: this test circuit is a **voltage divider**. When you use this technique, the voltmeter itself makes up half of the divider. The voltage across the leakage resistor cannot be measured directly, so we calculate it using Kirchhoff's Voltage Law by subtracting our voltmeter's reading from the voltage of our DC supply.

$$V_L = V_{in} - V_M$$

The current through the voltmeter's resistance is given by Ohm's Law.

$$I_M = \frac{V_M}{R_M}$$

The current through the leakage resistor is given by Ohm's Law.

$$I_L = \frac{V_L}{R_L}$$

We already determined that I_M and I_L are equal, so we can set the two previous expressions equal to each other.

$$I_M = I_L \Rightarrow \frac{V_M}{R_M} = \frac{V_L}{R_L}$$

We will rearrange the above equation to give an expression for R_L .

$$R_L = R_M \frac{V_L}{V_M}$$

Now we can substitute our first expression for V_L into the previous equation to eliminate V_M (the final unknown term).

$$R_L = R_M \frac{V_{in} - V_M}{V_M}$$

Rewriting the equation, the final result is

$$R_L = R_M \left(\frac{V_{in}}{V_M} - 1 \right)$$

To measure leakage current with a voltmeter, simply divide the meter's reading by the resistance of the meter. For example, if your $10\text{ M}\Omega$ voltmeter measures 0.023 V , then $I_{leakage} = 23\text{ mV}/10\text{ M}\Omega = 2.3\text{ nA}$. The accuracy of such a measurement depends both on the accuracy of the voltage measurement, and the tolerance of the meter's resistance.

Exercise 1.10


- (a) With two equal-value resistors, the output voltage is half the input voltage.

$$V_{\text{out}} = \frac{1}{2} V_{\text{in}} = \frac{30 \text{ V}}{2} = \boxed{15 \text{ V}}$$

- (b) To treat R_2 and R_{load} as a single resistor, combine the two resistors which are in parallel to find that the combined (equivalent) resistance is $5 \text{ k}\Omega$. Now, we have a simple voltage divider with a $10 \text{ k}\Omega$ resistor in series with the $5 \text{ k}\Omega$ equivalent resistor. The output voltage is across this equivalent resistance. The output voltage is given by


$$V_{\text{out}} = V_{\text{in}} \frac{5 \text{ k}\Omega}{10 \text{ k}\Omega + 5 \text{ k}\Omega} = \frac{30 \text{ V}}{3} = \boxed{10 \text{ V}}$$

Figure 1.11: Voltage divider with simplified equivalent resistance

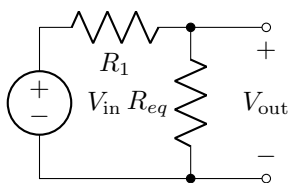

- (c) We can redraw the voltage divider circuit to make the “port” clearer.


Figure 1.12: Voltage divider with port shown.

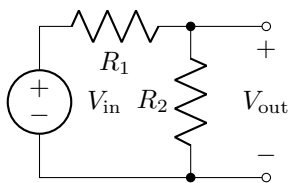

We can find V_{Th} by leaving the ports open (open circuit) and measuring V_{out} , the voltage across R_2 . This comes out to be half the input voltage when $R_1 = R_2$, so $V_{\text{out}} = 15 \text{ V}$. Thus $V_{\text{Th}} = \boxed{15 \text{ V}}$.

To find the Thévenin resistance, we need to find the short circuit current, I_{SC} . We short circuit the port and measure the current flowing through it.

Figure 1.13: Voltage divider with short circuit on the output.

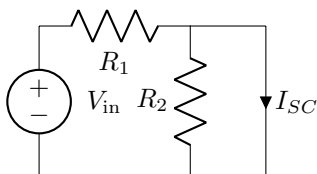


In this circuit, no current flows through R_2 , flowing through the short instead. Thus we have $I_{SC} = \frac{V_{in}}{R_1}$.

From this, we can find R_{Th} from $R_{Th} = \frac{V_{Th}}{I_{SC}}$. This gives us

$$R_{Th} = \frac{V_{Th}}{I_{SC}} = \frac{V_{Th}}{V_{in}/R_1} = \frac{15 \text{ V}}{30 \text{ V}/10 \text{ k}\Omega} = \boxed{5 \text{ k}\Omega}$$

The Thévenin equivalent circuit takes the form shown below.


Figure 1.14: Thévenin equivalent circuit.

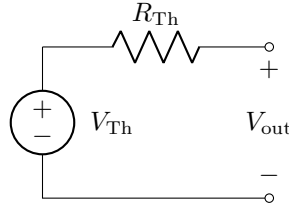

In terms of behavior at the ports, this circuit is equivalent to the circuit in Figure 1.11.

- (d) We connect the $10 \text{ k}\Omega$ load to the port of the Thévenin equivalent circuit in Figure 1.14 to get the following circuit.

Figure 1.15: Thévenin equivalent circuit with $10 \text{ k}\Omega$ load.

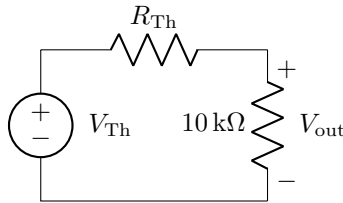


From here, we can find V_{out} , treating this circuit as a voltage divider.

$$V_{out} = \frac{10 \text{ k}\Omega}{R_{Th} + 10 \text{ k}\Omega} V_{Th} = \frac{10 \text{ k}\Omega}{5 \text{ k}\Omega + 10 \text{ k}\Omega} \cdot 15 \text{ V} = \boxed{10 \text{ V}}$$

This is the same answer we got in part (b).

- (e) To find the power dissipated in each resistor, we return to the original three-resistor circuit.

Figure 1.16: Original voltage divider with $10 \text{ k}\Omega$ load attached.

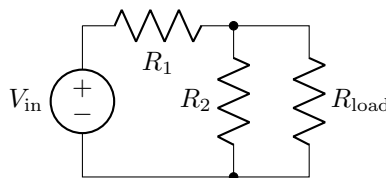

From part (d), we know that the output voltage is 10V and that this is the voltage across the load resistor. Since $P = IV = \frac{V^2}{R}$, we find that the power through R_{load} is

$$P_{\text{load}} = \frac{V^2}{R_{\text{load}}} = \frac{(10 \text{ V})^2}{10 \text{ k}\Omega} = \boxed{10 \text{ mW}}$$

Similarly, we know that the power across R_2 is the same since the voltage across R_2 is the same as the voltage across R_{load} . Thus we have

$$P_2 = \boxed{10 \text{ mW}}$$

To find the power dissipated in R_1 , we first have to find the voltage across it. From Kirchoff's loop rule, we know that the voltage around any closed loop in the circuit must be zero. We can choose the loop going through the voltage source, R_1 , and R_2 . The voltage supplied by the source is 30V. The voltage dropped across R_2 is 10V as discussed before. Thus the voltage dropped across R_1 must be $30 \text{ V} - 10 \text{ V} = 20 \text{ V}$. Now we know the voltage across and the resistance of R_1 . We use the same formula as before to find the power dissipated.

$$P_1 = \frac{V^2}{R_1} = \frac{(20 \text{ V})^2}{10 \text{ k}\Omega} = \boxed{40 \text{ mW}}$$

Exercise 1.11

Consider the following Thévenin circuit where R_{source} is just another name for the Thévenin resistance, R_{Th} .

Figure 1.17: Standard Thévenin circuit with attached load.



We will first calculate the power dissipated in the load and then maximize it with calculus. We can find the power through a resistor using current and resistance since $P = IV = I(IR) = I^2R$. To find the total current flowing through the resistors, we find the equivalent resistance which is $R_{\text{source}} + R_{\text{load}}$. Thus the total current flowing is $I = \frac{V_{\text{Th}}}{R_{\text{source}} + R_{\text{load}}}$. The power dissipated in R_{load} is thus

$$P_{\text{load}} = I^2 R_{\text{load}} = \frac{V_{\text{Th}}^2 R_{\text{load}}}{(R_{\text{source}} + R_{\text{load}})^2}$$

To maximize this function, we take the derivative and set it equal to 0.

$$\begin{aligned} \frac{dP_{\text{load}}}{dR_{\text{load}}} &= V_{\text{Th}} \frac{(R_{\text{source}} + R_{\text{load}})^2 - 2R_{\text{load}}(R_{\text{source}} + R_{\text{load}})}{(R_{\text{source}} + R_{\text{load}})^4} = 0 \\ \implies R_{\text{source}} + R_{\text{load}} &= 2R_{\text{load}} \\ \implies R_{\text{source}} &= R_{\text{load}} \end{aligned}$$

Exercise 1.12

(a) Voltage ratio: $\frac{V_2}{V_1} = 10^{\text{dB}/20} = 10^{3/20} = \boxed{1.413}$

Power ratio: $\frac{P_2}{P_1} = 10^{\text{dB}/10} = 10^{3/10} = \boxed{1.995}$

(b) Voltage ratio: $\frac{V_2}{V_1} = 10^{\text{dB}/20} = 10^{6/20} = \boxed{1.995}$

Power ratio: $\frac{P_2}{P_1} = 10^{\text{dB}/10} = 10^{6/10} = \boxed{3.981}$

(c) Voltage ratio: $\frac{V_2}{V_1} = 10^{\text{dB}/20} = 10^{10/20} = \boxed{3.162}$

Power ratio: $\frac{P_2}{P_1} = 10^{\text{dB}/10} = 10^{10/10} = \boxed{10}$

(d) Voltage ratio: $\frac{V_2}{V_1} = 10^{\text{dB}/20} = 10^{20/20} = \boxed{10}$

Power ratio: $\frac{P_2}{P_1} = 10^{\text{dB}/10} = 10^{20/10} = \boxed{100}$

Exercise 1.13

There are two important facts to notice from Exercise 1.12:

1. An increase of 3 dB corresponds to doubling the power
2. An increase of 10 dB corresponds to 10 times the power.

Using these two facts, we can fill in the table. Start from 10 dB. Fill in 7 dB, 4 dB, and 1 dB using fact 1. Then fill in 11 dB using fact 2. Then fill in 8 dB, 5 dB, and 2 dB using fact 1 and approximating 3.125 as π .

dB	ratio(P/P_0)
0	1
1	$\boxed{1.25}$
2	$\boxed{\pi/2}$
3	2
4	$\boxed{2.5}$
5	$\boxed{3.125 \approx \pi}$
6	4
7	$\boxed{5}$
8	$\boxed{6.25}$
9	8
10	10
11	$\boxed{12.5}$

Exercise 1.14

Recall the relationship between I , V , and C : $I = C \frac{dV}{dt}$. Now, we perform the integration:

$$\begin{aligned}\int dU &= \int_{t_0}^{t_1} V I dt \\ U &= \int_{t_0}^{t_1} C V \frac{dV}{dt} dt \\ &= C \int_0^{V_f} V dV \\ U &= \frac{1}{2} C V_f^2\end{aligned}$$

Exercise 1.15

Consider the following two capacitors in series.

Figure 1.18: Two capacitors in series.



To prove the capacitance formula, we need to express the total capacitance of both of these capacitors in terms of the individual capacitances. From the definition of capacitance, we have

$$C_{\text{total}} = \frac{Q_{\text{total}}}{V_{\text{total}}}$$

Notice that V_{total} is the sum of the voltages across C_1 and C_2 . We can get each of these voltages using the definition of capacitance.

$$V_{\text{total}} = V_1 + V_2 = \frac{Q_1}{C_1} + \frac{Q_2}{C_2}$$

The key observation now is that because the right plate of C_1 is connected to the left plate of C_2 , the charge stored on both plates must be of equal magnitude.³ Therefore, we have $Q_1 = Q_2$. Let us call this charge stored Q (i.e. $Q = Q_1 = Q_2$). Now, we know that the total charge stored is also Q .⁴ Therefore, we know that $Q_{\text{total}} = Q$. Now, we have

$$C_{\text{total}} = \frac{Q_{\text{total}}}{V_{\text{total}}} = \frac{Q}{Q_1/C_1 + Q_2/C_2} = \frac{Q}{Q/C_1 + Q/C_2} = \frac{1}{1/C_1 + 1/C_2}$$

³If this were not true, then there would be a net charge on these two plates and the wire between them. Because we assume that the capacitors started out with no net charge and there is no way for charge to leave the middle wire or the two plates it connects, this is impossible.

⁴If you are having trouble seeing this, suppose we apply a positive voltage to the left plate of C_1 relative to the right plate of C_2 . Suppose this causes the left plate of C_1 to charge to some charge q . We now must have a charge of $-q$ on the right plate of C_1 because q units of charge are now pushed onto the left plate of C_2 . Now the left of C_2 has q units of charge which causes a corresponding $-q$ charge on the right side of C_2 . Thus the overall total charge separated across these two capacitors is q .

Exercise 1.16

Equation 1.21 gives us the relationship between the time and the voltage (V_{out}) across the capacitor while charging. To find the rise time, subtract the time it takes to reach 10% of the final value from the time it takes to reach 90% of the final value.

$$V_{\text{out}} = 0.1V_f = V_f(1 - e^{-t_1/RC})$$

$$0.1 = 1 - e^{-t_1/RC}$$

$$t_1 = -RC \ln(0.9)$$


Similarly, we find that $t_2 = -RC \ln(0.1)$. Subtracting these two gives us

$$t_2 - t_1 = -RC(\ln(0.1) - \ln(0.9)) = 2.2RC$$

Exercise 1.17

The voltage divider on the left side of the circuit can be replaced with the Thévenin equivalent circuit found Exercise 1.10 (c). Recall that $V_{\text{Th}} = \frac{1}{2}V_{\text{in}}$ and $R_{\text{Th}} = 5 \text{ k}\Omega$. This gives us the following circuit.


Figure 1.19: Thévenin equivalent circuit to Figure 1.36 from the textbook.

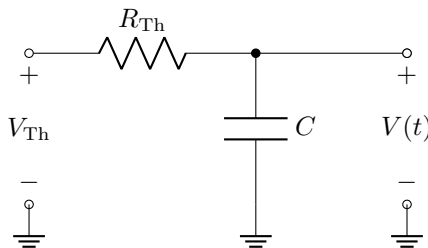

Now we have a simple RC circuit which we can apply Equation 1.21 to. The voltage across the capacitor is given by

$$V(t) = V_{\text{final}}(1 - e^{-t/RC}) = V_{\text{Th}}(1 - e^{-t/R_{\text{Th}}C}) = \boxed{\frac{1}{2}V_{\text{in}}(1 - e^{-t/(5 \times 10^{-4})})}$$

Figure 1.20: $V(t)$ sketch.

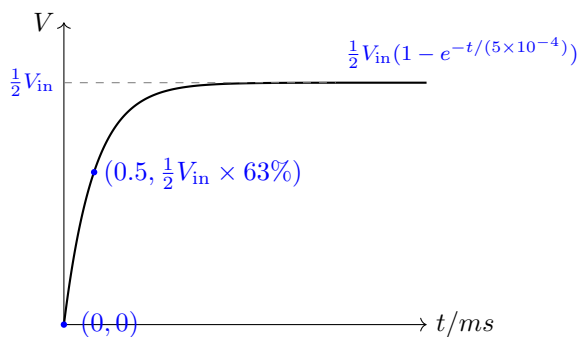

Exercise 1.18

From the capacitor equation in the previous paragraph, we have

$$V(t) = (I/C)t = (1 \text{ mA}/1 \text{ }\mu\text{F}) \times t = 10 \text{ V}$$

This gives us

$$t = 0.01 \text{ s}$$

Exercise 1.19

Suppose a current I is flowing through a loop of wire with cross-sectional area A . This induces a magnetic field B , and the flux Φ through the loop is

$$\Phi = BA$$

Now suppose the same current I flows through a wire coiled into n loops, each with the same cross-sectional area A . This induces a magnetic field of n times the strength, $B_n = nB$. Since each loop has area A , the total cross-sectional area of the coil can be considered $A_n = nA$. Then the magnetic flux through the coil is

$$\Phi_n = B_n A_n = n^2 BA = n^2 \Phi$$

Since inductance is defined as flux through a coil divided by current through the flux, we can see that $\Phi_n = n^2 \Phi$ implies $L \propto n^2$.

Exercise 1.20

We can use the formula for the full-wave rectifier ripple voltage to find the capacitance.

$$\frac{I_{\text{load}}}{2fC} = \Delta V \leq 0.1 V_{\text{p-p}}$$

The maximum load current is 10mA and assuming a standard wall outlet frequency of 60 Hz, we have

$$C \geq \frac{10 \text{ mA}}{2 \times 60 \text{ Hz} \times 0.1 \text{ V}} = 833 \text{ }\mu\text{F}$$

Now we need to find the AC input voltage. The peak voltage after rectification must be 10 V (per the requirements). Since each phase of the AC signal must pass through 2 diode drops, we have to add this to find out what our AC peak-to-peak voltage must be. Thus we have

$$V_{\text{in,p-p}} = 10 \text{ V} + 2(0.6 \text{ V}) = 11.2 \text{ V}$$

Exercise 1.21

In order to calculate the minimum fuse rating for a time-varying current signal, one must calculate the RMS current of the signal - *not* the average current. This is because most fuses are designed to blow at a certain average power level, and average power is related to the average of the *square* of current.

Square waves are defined by two amplitudes. When one of those amplitudes is zero, the RMS value is given by the following equation:

$$I_{\text{RMS}} = \sqrt{\frac{I^2 + 0}{2}} = \sqrt{\frac{I^2}{2}} = \frac{I}{\sqrt{2}}$$


So in the case of a 0 to 2.0 A square wave with 50% duty cycle, the theoretical minimum current a fuse should be rated for is:

$$\frac{I}{\sqrt{2}} = \frac{2}{\sqrt{2}} = \boxed{\sqrt{2}A}$$

In this case, sizing a fuse for the *average* current (1 A) would too small by a factor of $\sqrt{2}$!

Exercise 1.22


Figure 1.21: A symmetric 5.6 V clamping circuit.

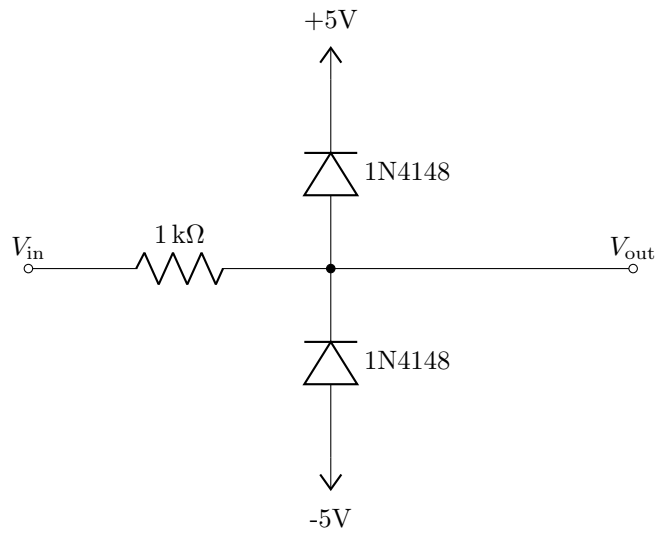

Exercise 1.23

For both low-pass and high-pass filters of the first-order, the **input** impedance is calculated by the series combination of impedances of both circuit elements. The **output** impedance is calculated as the parallel combination of the impedances of the two circuit elements.

Figure 1.22: Low-Pass Filter Driven by a Voltage Source.

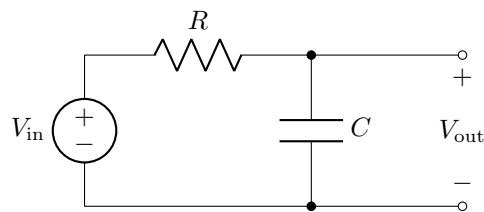


The minimum input impedance of a low-pass filter occurs at high frequency when the capacitor looks like a short circuit. This is true because this minimizes the impedance of the series-combination of impedances.

$$\boxed{Z_{\text{in,min}} = R + 0 = R}$$

The maximum output impedance a low-pass filter occurs at low frequency when the capacitor looks like an open circuit. This is true because this maximizes the impedance of the parallel-combination of impedances.

$$Z_{\text{out,max}} = R \parallel \infty = R$$

Figure 1.23: High-Pass Filter Driven by a Voltage Source.

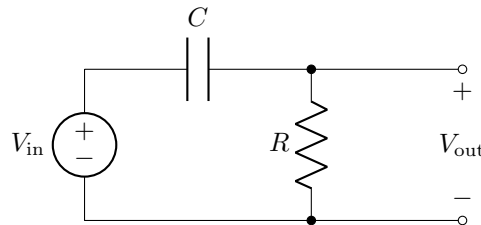


The reasoning for the high-pass filter is the same as for the low-pass filter. The circuit elements are swapped in their position, but the analysis is the same because: minimizing the input impedance is still a function of minimizing the series combination impedance; maximizing the output impedance is still a function of maximizing the parallel combination impedance.

Exercise 1.24

As the question indicated, the bandpass filter is made of a highpass filter and lowpass filter as shown below.

Figure 1.24: Bandpass filter

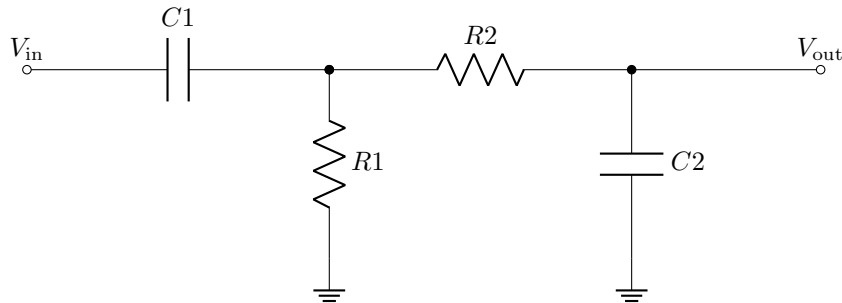

For highpass and lowpass filters, we have

$$f_{3\text{dB}} = \frac{1}{2\pi * RC}$$

Given breakpoints, we can determine the resistors and capacitors values to meet the design requirements.

(a) Given $f_1 = 100 \text{ Hz}$ from the question:

$$R_1 * C_1 = \frac{1}{2\pi * 100 \text{ Hz}} = 1.6 \text{ ms}$$

Because the signal source output impedance is 100Ω , we select a value 10 times higher: $R_1 = 1\text{ k}\Omega$ then:

$$C_1 = \frac{1.6\text{ ms}}{1\text{ k}\Omega} = \boxed{1.6\text{ }\mu\text{F}}$$

(b) Given $f_2 = 10\text{ kHz}$ from the question:

$$R_2 * C_2 = \frac{1}{2\pi * 10\text{ kHz}} = 16\text{ }\mu\text{s}$$

Because the output impedance of the high-pass filter was approximately $1\text{ k}\Omega$, we select a value 10 times greater: $R_2 = 10\text{ k}\Omega$ then:

$$C_2 = \frac{16\text{ }\mu\text{s}}{10\text{ k}\Omega} = \boxed{1.6\text{ nF}}$$

Exercise 1.25

(a) The impedance of 2 parallel capacitors is equal to the impedance of a single capacitor C of value $C_1 + C_2$:

$$\mathbf{Z}_{\text{parallel}} = \frac{1}{\frac{1}{\mathbf{Z}_1} + \frac{1}{\mathbf{Z}_2}} = \frac{1}{j\omega C_1 + j\omega C_2} = \boxed{\frac{1}{j\omega(C_1 + C_2)}}$$

(b) The impedance of 2 series capacitors is equal to the impedance of a single capacitor C of value $\frac{C_1 C_2}{C_1 + C_2}$:

$$\begin{aligned} \mathbf{Z}_{\text{series}} &= \mathbf{Z}_1 + \mathbf{Z}_2 \\ &= \frac{1}{j\omega C_1} + \frac{1}{j\omega C_2} \\ &= \frac{1}{j\omega} \left(\frac{1}{C_1} + \frac{1}{C_2} \right) \\ &= \frac{1}{j\omega} \left(\frac{C_2}{C_1 C_2} + \frac{C_1}{C_2 C_1} \right) \\ &= \frac{1}{j\omega} \left(\frac{C_1 + C_2}{C_1 C_2} \right) \\ &= \frac{1}{j\omega} \frac{1}{\left(\frac{C_1 C_2}{C_1 + C_2} \right)} \\ &= \boxed{\frac{1}{j\omega \left(\frac{C_1 C_2}{C_1 + C_2} \right)}} \end{aligned}$$

Exercise 1.26

$$Ae^{j\theta} = Be^{j\phi}Ce^{j\alpha} = BCe^{j(\phi+\alpha)}$$

Therefore, because A , B , and C are all real numbers, θ must be equal to $(\phi + \alpha)$, so the exponentials on either side of the equation cancel.

$$Ae^{j\theta} = BCe^{j(\phi+\alpha)}$$

$$Ae^{j\theta} = BCe^{j\theta}$$

$$\boxed{A = BC}$$

Exercise 1.27

We can solve this problem from two approaches: analitically, or by inspecting the power waveform over a full cycle. First analytically:

$$V(t) = V_0 \cos(2\pi ft)$$

$$I(t) = I_0 \cos\left(2\pi ft + \frac{\pi}{2}\right)$$

Define the voltage

and current waveforms

$$P(t) = V(t) \cdot I(t)$$

$$= V_0 I_0 \cos(2\pi ft) \cos\left(2\pi ft + \frac{\pi}{2}\right)$$

Using cosine multiplication rule

$$= V_0 I_0 \frac{\cos\left(4\pi ft + \frac{\pi}{2}\right) + \cancel{\cos\left(\frac{\pi}{2}\right)}}{2} \rightarrow 0$$

we express the power waveform

as a sum of two cosines

$$P_{\text{av}} = \frac{1}{T} \int_0^T V_0 I_0 \frac{\cos\left(4\pi ft + \frac{\pi}{2}\right)}{2} dt$$


From this point we take the integral

$$= \frac{V_0 I_0}{2T} \left[\frac{\sin\left(4\pi ft + \frac{\pi}{2}\right)}{4\pi f} \right]_{t=0}^{t=T}$$

and evaluate over one cycle

$$= \frac{V_0 I_0}{8\pi} \underbrace{\left(\sin\left(4\pi + \frac{\pi}{2}\right) - \sin\left(\frac{\pi}{2}\right) \right)}_{1-1=0} = \boxed{0}$$

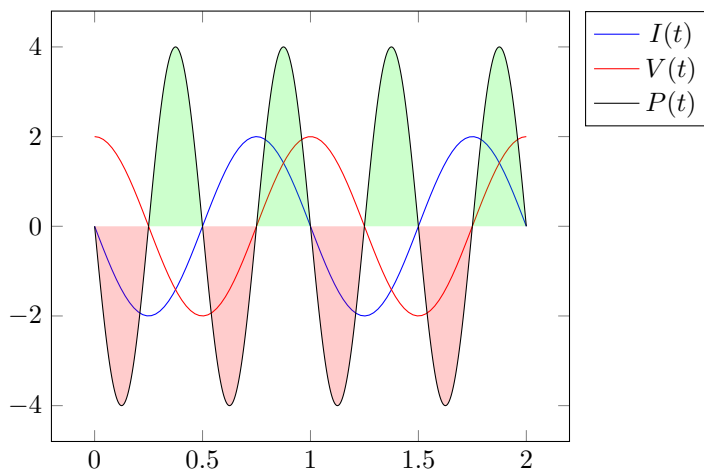
As an alternative method we can avoid the integration part by simply observing the power waveform over one full cycle considering $f = 1$, $I_0 = V_0 = 2$



From the plot it is clear that the red and green areas are equal and opposite and thus when integrating over a integer number of cycles the average power will be zero.

Exercise 1.28

Figure 1.25: RC Circuit with AC Voltage Source

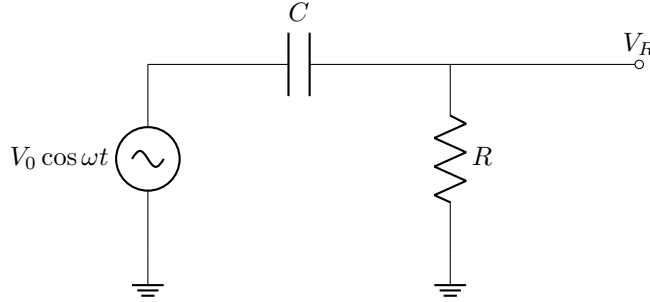

From discussions before this question, we know that

$$P = \text{Re}(VI^*) = \frac{V_0^2 R}{R^2 + (\frac{1}{\omega^2 C^2})} = \frac{V_0^2}{R} * \frac{(\omega RC)^2}{1 + (\omega RC)^2}$$

Since R and C are connected in series, we have

$$\frac{V_R}{V_0} = \frac{R}{R + \frac{1}{j\omega C}}$$

Thus, we can calculate the power consumed by the resistor in the following steps.

$$V_R = V_0 * \frac{j\omega RC}{1 + j\omega RC}$$

$$\frac{V_R^2}{R} = \frac{V_0^2}{R} * \frac{(\omega RC)^2}{1 + (\omega RC)^2}$$

We can see that it is equal to the real power delivered to the circuit. In another word, all the real power delivered to this circuit is consumed in the resistor.

Exercise 1.29

(a) RLC series circuit

Since the resistor, inductor, and capacitor are in series, we can calculate the impedance of the circuit by adding individual impedance together.

$$Z = R + j\omega L - j\frac{1}{\omega C}$$

Given $C = \frac{1}{\omega^2 L}$,

$$Z = R + j\omega L - j\omega L = R$$

Thus, this reactive circuit can be treated as a resistive circuit when calculating the power factor, which is 1.

(b) RLC parallel circuit

Since all the components are in parallel, the invert of total impedance is the sum of inverts of all components' impedance

$$\frac{1}{Z} = \frac{1}{R} + \frac{1}{j\omega L} + j\omega C$$

Given $C = \frac{1}{\omega^2 L}$,

$$\frac{1}{Z} = \frac{1}{R} + \frac{1}{j\omega L} - \frac{1}{j\omega L} = \frac{1}{R}$$

Similarly, this show that this circuit can also be treated as a resistive circuit whoes power factor is 1.

Exercise 1.30

V_{out} is simply the voltage at the output of an impedance voltage divider. We know that $Z_R = R$ and $Z_C = \frac{1}{j\omega C}$. Thus we have

$$V_{\text{out}} = \frac{Z_C}{Z_R + Z_C} V_{\text{in}} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} V_{\text{in}} = \frac{1}{1 + j\omega RC} V_{\text{in}}$$

The magnitude of this expression can be found by multiplying by the complex conjugate and taking the square root.

$$\sqrt{V_{\text{out}} V_{\text{out}}^*} = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}} V_{\text{in}}$$

Exercise 1.31

From the frequency response of lowpass filter plotted on logarithmic axes, we know

$$\phi = -\arctan\left(\frac{f}{f_c}\right)$$

Thus, when $f = 0.1f_{3\text{dB}}$,

$$\phi = -\arctan(0.1) \approx -5.71^\circ \approx -6^\circ$$

Similarly, when $f = 10f_{3\text{dB}}$,

$$\phi = -\arctan(10) \approx -84.29^\circ$$

The phase shift can also be expressed as $-(-90 - (-84.29)) \approx 5.71^\circ \approx 6^\circ$

In summary, for single-section RC filters, the phase shift is $\approx 6^\circ$ from its asymptotic value at $0.1f_{3\text{dB}}$ and $10f_{3\text{dB}}$.

Exercise 1.32

Given that the current is the same everywhere in series circuits, the axes also shows the relationships among voltages.

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{R}{\text{hypotenuse}}$$

By Pythagorean Theorem,

$$\frac{R}{\text{hypotenuse}} = \frac{R}{\sqrt{R^2 + (-j/\omega C)^2}} = \frac{R}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}}$$

Thus, $V_{\text{out}} = V_{\text{in}} * \frac{R}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}}$

Exercise 1.33

For the lowpass filter, V_{out} and V_{in} have the following relationship.

$$V_{\text{out}} = V_{\text{in}} * \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$

Given $V_{\text{out}} = \frac{1}{2} V_{\text{in}}$,

$$\frac{1}{\sqrt{1 + \omega^2 R^2 C^2}} = \frac{1}{2}$$

Thus, solving for ω

$$\frac{1}{1 + \omega^2 R^2 C^2} = \frac{1}{4}$$

$$1 + \omega^2 R^2 C^2 = 4$$

$$\omega^2 R^2 C^2 = 3$$

$$\omega = \frac{\sqrt{3}}{RC}$$

Since $f = \frac{\omega}{2\pi}$,

$$f = \frac{\sqrt{3}}{2\pi RC}$$

From previous calculation, we have $C = \frac{\sqrt{3}}{RC}$ From the phasor diagram for lowpass filter at $3dB$ point, we know that

$$\angle = \arctan\left(\frac{-j}{R}\right) = \arctan\left(-\frac{1}{\sqrt{3}}\right) = -30^\circ$$

Thus, the phase shift is

$$\phi = -90^\circ - (-30^\circ) = -60^\circ$$

Exercise 1.34

From the phasor diagram, we can see that

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{C}{\text{hypotenuse}} = \frac{C}{\sqrt{R^2 + C^2}}$$

plugging in $C = \frac{-j}{\omega C}$

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{\frac{-j}{\omega C}}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}} = \frac{-j}{\omega C} * \frac{\omega C}{\sqrt{R^2 \omega^2 C^2 + 1}} = \frac{-j}{\sqrt{R^2 \omega^2 C^2 + 1}}$$

Exercise 1.35

Resistor, inductor, and capacitor in series forms a voltage divider, so

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{Z_{LC}}{R + Z_{LC}}$$

Since the inductor and capacitor are in series and $\omega_0 = \frac{1}{\sqrt{LC}}$, which was derived from $f_0 = \frac{1}{2\pi\sqrt{LC}}$. We can write Z_{LC} as following,

$$Z_{LC} = Z_L + Z_C = j\omega L + \frac{-j}{\omega C} = j\left(\omega L - \frac{1}{\omega C}\right) = jL\left(\frac{\omega^2 - \omega_0^2}{\omega}\right)$$

We can describe the response in the following conditions:

- (a) When $f = f_0$, $\omega = \omega_0$ and $Z_{LC} = 0$. Thus, $\frac{V_{out}}{V_{in}} = 0$.
- (b) When $f < f_0$, $\omega < \omega_0$ and $Z_C > Z_L$, which makes the circuit more capacitive. Thus, the circuit has a similar response as capacitors.
- (c) When $f > f_0$, $\omega > \omega_0$ and $Z_L > Z_C$, which means the inductor has more impact on the general response of the whole circuit. Thus, the circuit responses more like inductors.

Thus, we see the response plot captured in Figure 1.109 from the textbook.

Exercise 1.36

We can see from textbook Figure 1.122 that two SPDT switches can control the lamp independently. We need to explore wirings that allow DPDT switches to switch from two states. The following wire shows how to turn DPDT switches to work as described.

Figure 1.26: Wiring a DPDT switch to switch from two states


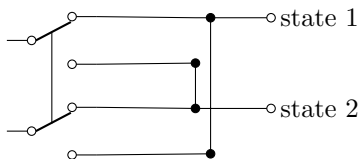



Figure 1.27: Generalization of “three-way” Switch Wiring with Two SPDT Switches And $N - 2$ DPDT Switches

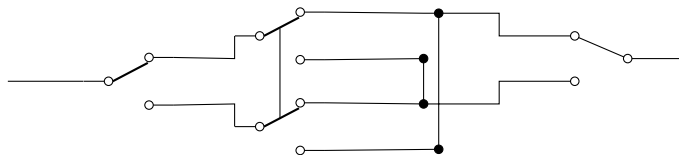


Exercise 1.37

Recall that $I_{Norton} = I_{short \text{ circuit the load}}$, so we can transform the circuit as shown below.


Figure 1.28: Circuit to find I_{Norton}

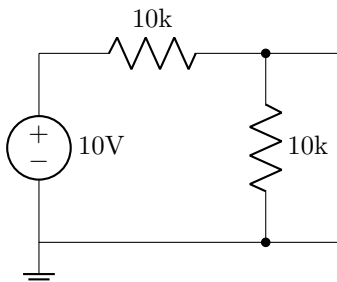

Then, $I_{\text{Norton}} = \frac{10\text{V}}{10\text{k}\Omega} = 1\text{mA}$ To find R_{Norton} , it's very similar to how we find R in superposition where we remove all power sources. Then, the circuit is transformed as shown below.

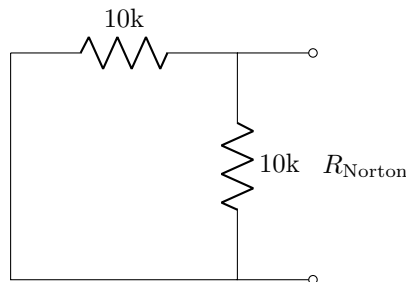
Figure 1.29: Circuit to find R_{Norton} 

Based on the circuit, $R_{\text{Norton}} = \frac{1}{\frac{1}{10} + \frac{1}{10}} = 5\text{k}\Omega$ Thus, the Norton equivalent circuit is shown below.

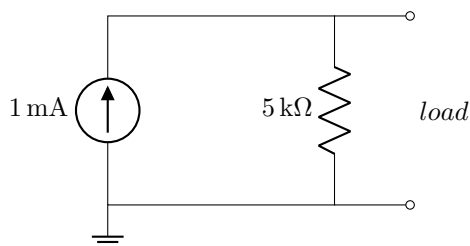Figure 1.30: Circuit to find R_{Norton} 

When the $R_{\text{load}} = 5\text{k}\Omega$, $V_{\text{out}} = \frac{5\text{k}\Omega}{2} * 1\text{mA} = 2.5\text{V}$ And, the original circuit is as shown below.

Figure 1.31: Original Circuit with a 5kΩ load

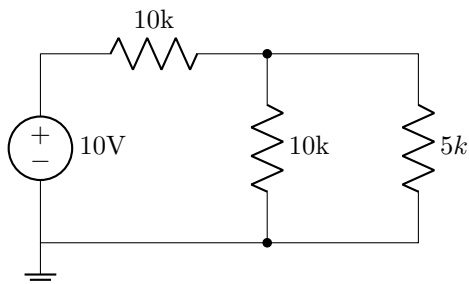

Thus, $V_{\text{out}} = \frac{V_{\text{in}} * \frac{1}{\frac{1}{10} + \frac{1}{5}}}{10 + \frac{1}{\frac{1}{10} + \frac{1}{5}}} = 2.5\text{V}$

Finally, we showed that the Norton equivalent gives the same output voltage as the actual circuit when loaded by a 5k resistor.

Exercise 1.38

Based on the circuit shown in this exercise, $V_{Th} = V_{open} = 0.5 \text{ mA} * 10 \text{ k}\Omega = 5 \text{ V}$

$$I_{short} = 0.5 \text{ mA}, \text{ so } R_{Th} = \frac{5 \text{ V}}{0.5 \text{ mA}} = 10 \text{ k}\Omega$$

Similarly, we can find the Thévenin equivalent for the previous exercise.

$$V_{Th} = \frac{10 \text{ k}\Omega}{10 + 10} * V_{in} = 5 \text{ V}$$

$$I_{short} = \frac{10 \text{ V}}{10 \text{ k}\Omega} = 1 \text{ mA}$$

$$R_{Th} = \frac{5 \text{ V}}{1 \text{ mA}} = 5 \text{ k}\Omega$$

Since the R_{Th} is different from the previous result, we can see that these Thévenin circuits are not the same.

Exercise 1.39

Based on the filter behaviors, the “rumble filter” is essentially a high-pass filter.

Given $f_{3dB} = 10 \text{ Hz}$ from the question:


$$R * C = \frac{1}{2\pi * 10 \text{ Hz}} \approx 16 \text{ ms}$$

Since the load ($10 \text{ k}\Omega$ minimum) is in parallel with the resistor in the RC high-pass filter, we should select a relatively small resistor for the filter design so that the load doesn't affect the filter's performance significantly. We select a resistor: $R = \frac{10 \text{ k}\Omega}{100} = 100 \Omega$ then:

$$C = \frac{16 \text{ ms}}{100 \Omega} = 160 \mu\text{F}$$

The filter design is shown below.

Figure 1.32: Rumble Filter

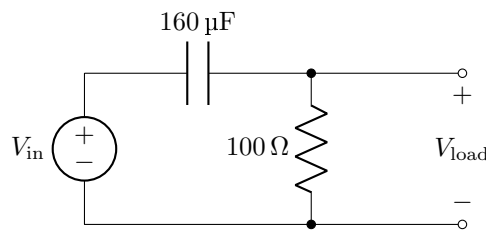

Exercise 1.40

The “scratch filter” for audio signals is essentially a low-pass filter that filter out high-frequency sounds, such as scratches.


Given $f_{3dB} = 10 \text{ kHz}$ from the question:

$$R * C = \frac{1}{2\pi * 10 \text{ kHz}} = 0.016 \text{ ms}$$

Similar to the high-pass filter design in the previous question, we need to pick a low impedance capacitor so that the load doesn't affect the filter's performance significantly. We select a capacitor: $C = 0.01 \mu\text{F}$ then:

$$R = \frac{1}{2\pi * 10000 * 0.01 * 0.000001} \approx 1.6 \text{ k}\Omega$$

Figure 1.33: Scratch Filter

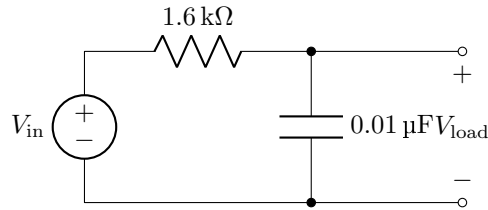

Exercise 1.41


Since we need to design a filter using resistors and capacitors to produce the results as plotted, we need to think of RC circuits that we discussed before as building blocks for this problem.

Based on the plot, when $\omega < \omega_0$, the filter acts like a voltage divider and $\frac{V_{out}}{V_{in}} = 0.5$

When $\omega > \omega_0$, the filter looks like a high-pass filter.

We can combine voltage divider circuit and high-pass filter as shown below.

Figure 1.34: High-emphasis filter

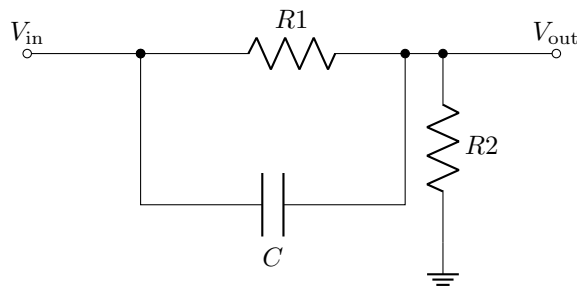


when $\omega < \omega_0$, the capacitor acts as if it's open, and the circuit is a voltage divider.

Given that $\frac{V_{out}}{V_{in}} = 0.5$, $R_1 = R_2 = R$

When $\omega > \omega_0$, the high frequency signals can pass the capacitor, but low frequency signals are blocked. We can find the capacitor value by treating the circuit as a high-pass filter. $f_{3dB} = \frac{1}{2\pi * RC}$ and $\omega = 2\pi * f_{3dB}$ so $C = \frac{R}{\omega_0}$

Exercise 1.42

Figure 1.35: Bandpass filter

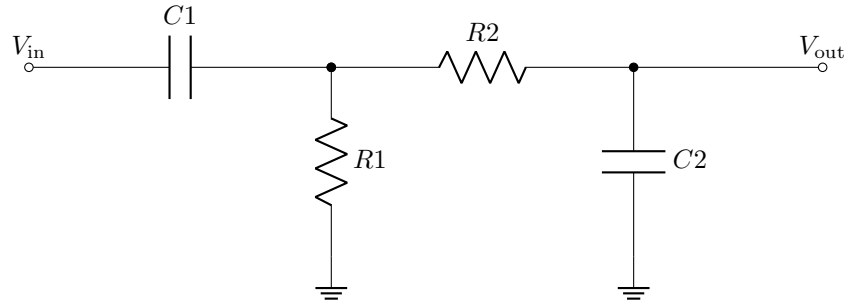

The bandpass filter is made of a high-pass filter and a low-pass filter. Thus, given f_1 and f_2 , we have

$$f_1 = \frac{1}{2\pi * R_1 * C_1}$$

$$f_2 = \frac{1}{2\pi * R_2 * C_2}$$

As discussed in the session “Driving and loading RC filters” in the book, the assumptions are small input impedance compared to the load. We can set $R_1 = \frac{1}{10} * R_2$, and then

$$C_2 = \frac{1}{2\pi * f_2 R_2}$$

$$C_1 = \frac{1}{f_1 * 2\pi R_1} = \frac{1}{f_1 * 2\pi * 0.1 R_2} = \frac{5}{\pi R_2 f_1}$$

Exercise 1.43

The circuit is the diode limiter discussed before (Figure 1.78 in the textbook), and the output is the same as the plots A and B in *Figure1.79*. We need to find the characters of the output signal. Given that $f = 60$ Hz

$$T = \frac{1}{f} = \frac{1}{60} \approx 17 \text{ ms}$$

$$\omega = 2\pi f = 120\pi$$


Exercise 1.44

The equivalent capacitance of the oscilloscope and cable is

$$C_o = 100 \text{ pF} + 20 \text{ pF} = 120 \text{ pF}$$

The equivalent input impedance of the oscilloscope and the total capacitance is: $Z_o = \left(R_o \parallel \frac{1}{j\omega C_o} \right)$ where R_o is the input resistance of the scope ($1 \text{ M}\Omega$). In order to reduce the voltage by a factor of 10, let us create a voltage divider between the probe tip and the equivalent scope-and-cable input impedance.

Figure 1.36: Basic Voltage Divider

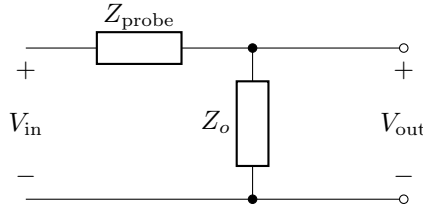

In order to reduce the voltage by a factor of ten, our circuit must satisfy

$$V_{out} = \frac{V_{in}}{10}$$

We know that the output of a voltage divider is given by

$$V_{out} = V_{in} \frac{Z_{out}}{Z_{out} + Z_{in}}$$

When we equate the previous two expressions, it yields

$$\frac{V_{in}}{10} = V_{in} \frac{Z_o}{Z_o + Z_{probe}}$$

We may cancel V_{in} from both sides of the equation and rearrange terms

$$Z_o + Z_{probe} = 10Z_o$$

Subtract Z_o from both sides to solve for the probe impedance:


$$\begin{aligned} Z_{probe} &= 9Z_o \\ &= 9 \left(R_o \parallel \frac{1}{j\omega C_o} \right) \\ &= 9R_o \parallel \frac{9}{j\omega C_o} \\ &= 9R_o \parallel \frac{1}{j\omega \left(\frac{1}{9}C_o \right)} \end{aligned}$$

So our “x10 probe” should be the parallel combination of a resistor and a capacitor. The resistor should be 9 times greater than the input resistance of the scope (R_o). The probe’s capacitor should be 9 times *smaller* than C_o (the total capacitance of the cable and the oscilloscope).

$$R_{probe} = 9R_o$$

$$C_{probe} = \frac{1}{9}C_o$$

Figure 1.37: x10 Probe

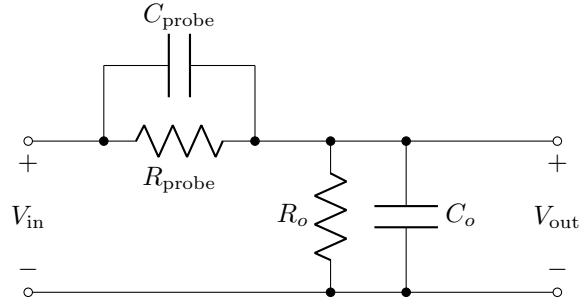

Many x10 probes implement C_{probe} as a variable capacitor that the user may tune to very near one ninth the cable-plus-oscilloscope capacitance. This is sometimes referred to as “probe compensation”.

The input impedance of this x10 probe is

$$\begin{aligned}
 Z_{in} &= Z_{probe} + Z_o \\
 &= 9R_o \parallel \frac{1}{j\omega \left(\frac{1}{9}C_o\right)} + \left(R_o \parallel \frac{1}{j\omega C_o}\right) \\
 &= 9 \left(R_o \parallel \frac{1}{j\omega C_o}\right) + \left(R_o \parallel \frac{1}{j\omega C_o}\right) \\
 &= 10 \left(R_o \parallel \frac{1}{j\omega C_o}\right) \\
 Z_{in} &= \boxed{10Z_o}
 \end{aligned}$$

Finally, lets take a look at how the probe and the oscilloscope (working as a voltage divider) affect the output voltage as a function of the input voltage.

$$\begin{aligned}
 \frac{V_{out}}{V_{in}} &= \frac{Z_o}{Z_{in}} \\
 &= \frac{R_o \parallel \frac{1}{j\omega C_o}}{10 \left(R_o \parallel \frac{1}{j\omega C_o}\right)} \\
 \frac{V_{out}}{V_{in}} &= \frac{1}{10}
 \end{aligned}$$

It is remarkable! The voltage transfer function of this circuit is *precisely* $\frac{1}{10}$. This circuit contains four passive components (two of them reactive) but **the transfer function does not depend on frequency**. Truly, the ancients were wise and knew many great things.

Solutions for Chapter 2

Exercise 2.1

In order to solve this problem, many assumptions must be made. Different people may assume slightly different values for parameters. This is OK. What is important is making good assumptions and checking our conclusions to make sure they are reasonable.

To solve for the current in the LED, let us assume we know the LED is red, so it follows the red LED curve from Figure 2.8 in the book. Let us also assume the transistor is acting like a closed switch, so the collector voltage of Q1 is close to 0 V. Let us also assume the LED is ON, so its voltage is approximately $V_{\text{LED}} = 2 \text{ V}$. From the preceding assumptions, we can calculate that the LED current is

$$I_{\text{LED}} = \frac{3.3 \text{ V} - 2 \text{ V}}{330 \Omega} = \frac{1.3 \text{ V}}{330 \Omega} \approx 3.94 \text{ mA}$$

If we use Figure 2.8 (from the textbook) to check our numbers, we see that a current of 3.94 mA roughly correlates to an LED voltage of $V_{\text{LED}} = 1.7 \text{ V}$. We will run the same calculation again to reduce our error.

$$I_{\text{LED}}^* = \frac{3.3 \text{ V} - 1.7 \text{ V}}{330 \Omega} = \frac{1.6 \text{ V}}{330 \Omega} \approx \boxed{4.85 \text{ mA}}$$

In order to determine the minimum current gain required from our transistor, we must calculate the base current. Let us assume we know the base-emitter voltage $V_{\text{BE}} = 0.6 \text{ V}$. Therefore


$$I_{\text{B}} = \frac{3.3 \text{ V} - 0.6 \text{ V}}{10 \text{ k}\Omega} = 270 \mu\text{A}$$

So the minimum current gain must be

$$\beta_{\text{min}} = \frac{I_{\text{LED}}^*}{I_{\text{B}}} \approx \frac{4.85 \text{ mA}}{270 \mu\text{A}} \approx \boxed{18.0}$$

Exercise 2.2

When Q_1 goes is in saturation, the base voltage of Q_2 equals the opposite of the voltage on the capacitor C_1 at $t = 0 \text{ s}$, $V_0 = 4.4 \text{ V}$ and Q_2 is then cutoff. V_{out} will be equal to 5 V until Q_2 is brought in saturation again. This happens when its base voltage gets higher or equal to the Q_2 threshold voltage (0.6 V). As soon as Q_1 is brought in saturation, C_1 starts to discharge into the resistor R_3 and the equivalent circuit, valid until Q_2 is cutoff, is then:

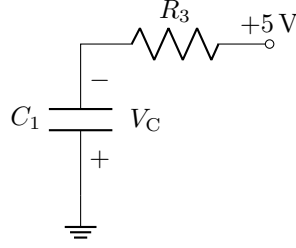Figure 2.1: Equivalent C_1 discharging circuit.

The time evolution of the voltage across the capacitor C_1 is given by:

$$V_C(t) = (V_0 - V_\infty) e^{-\frac{t}{R_3 C_1}} + V_\infty$$

where V_∞ is the steady-state voltage on the capacitor C_1 end equals -5 V . Given the considerations above, we have that $V_C(t = T_{\text{pulse}}) = -0.6\text{ V}$. Solving for t gives:

$$T_{\text{pulse}} = -R_3 C_1 \ln \left(\frac{-0.6\text{ V} - V_\infty}{V_0 - V_\infty} \right) = \boxed{0.76 R_3 C_1 = 76\text{ }\mu\text{s}}$$

Exercise 2.3

The output voltage is now influenced by R_5 that goes in series with R_4 , and by the V_{BE} of Q_3 which is equal to 0.6 V when the transistor is in saturation. Therefore:

$$V_{\text{out}} = \frac{R_5}{R_5 + R_4} (5\text{ V} - 0.6\text{ V}) + 0.6\text{ V} = \boxed{4.79\text{ V}}$$

The minimum value of β of Q_3 can be obtained looking at the maximum value of the current flowing through the collector of Q_3 , $I_c^{Q_3}$. As soon as Q_1 goes in saturation, the capacitor C_1 starts to discharge and its current is given by $C_1 dV_C/dt$. With reference to the variables introduced in the previous exercise (2.2):


$$I_c^{Q_3}(t) = \frac{5\text{ V}}{R_2} - I_{C_1}(t) = \frac{5\text{ V}}{R_2} + C_1 \frac{1}{R_3 C_1} (V_0 - V_\infty) e^{-\frac{t}{R_3 C_1}}$$

Therefore:

$$\beta_{\min} = \frac{I_c^{Q_3}(t)|_{\max}}{I_b^{Q_3}} = \frac{I_c^{Q_3}(t=0\text{ s})}{I_b^{Q_3}} = \boxed{27}$$

Exercise 2.4

Figure 2.2: Emitter follower circuit used for computing the output resistance

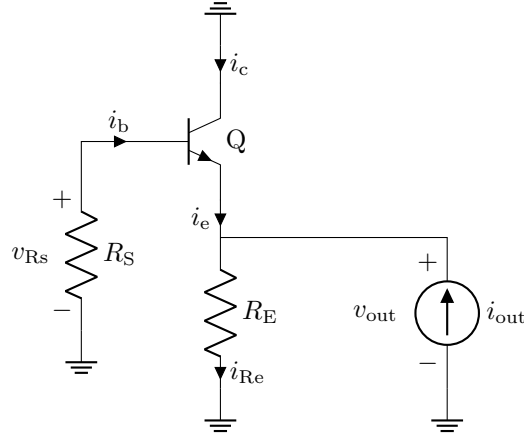

Applying the KCL on the Q transistor:

$$i_e = i_b + i_c = i_b (\beta + 1)$$

The current flowing through the emitter resistor R_E is equal to:

$$i_{Re} = i_e + i_{out} = i_b (\beta + 1) + i_{out}$$

Since for the emitter follower $v_{Rs} = v_{out}$:

$$[i_b (\beta + 1) + i_{out}] R_E = v_{out}$$

Since:

$$i_b = -\frac{v_{Rs}}{R_S} = -\frac{v_{out}}{R_S}$$

we can write:

$$\left[-\frac{v_{out}}{R_S} (\beta + 1) + i_{out} \right] R_E = v_{out}$$

Therefore:


$$R_{out} = \frac{v_{out}}{i_{out}} = \frac{R_E R_S}{R_S + (\beta + 1) R_E}$$

If $R_E \gg R_S/(\beta + 1)$:

$$R_{out} \approx \frac{R_S}{(\beta + 1)}$$


Exercise 2.5

Figure 2.3: Small signal circuit

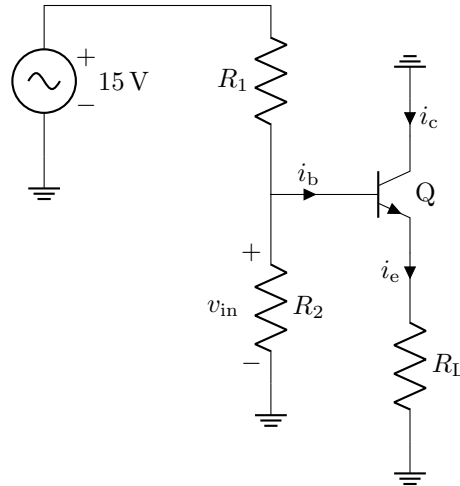

In order to achieve a maximum voltage change of 5% for a maximum current to the load (R_L) equal to 25 mA, we can make reference to the equivalent circuit of Figure 2.4:

Figure 2.4: Output equivalent circuit

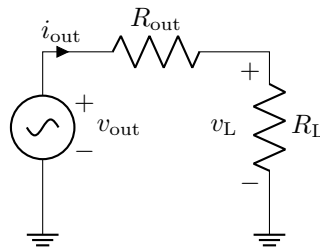

obtaining:

$$\left. \frac{v_{\text{out}} - v_L}{v_{\text{out}}} \right|_{i_{\text{out}}=25 \text{ mA}} = 0.05$$

Since

$$v_{\text{out}} - R_{\text{out}} i_{\text{out}} = v_L$$

and for an emitter follower $v_{\text{out}} = v_{\text{in}} = 5 \text{ V}$ we can write:

$$\frac{R_{\text{out}} 25 \text{ mA}}{5 \text{ V}} = 0.05$$

obtaining the following condition on R_{out} :

$$R_{\text{out}} = \frac{0.05 \cdot 5 \text{ V}}{25 \text{ mA}}$$

For the emitter follower configuration:

$$R_{\text{out}} = \frac{R_{\text{in}}}{\beta + 1}$$

and we see from the circuit of Figure 2.3 that R_{in} is given by the parallel between R_1 and R_2 :

$$R_{\text{in}} = \frac{R_1 R_2}{R_1 + R_2}$$

In order to achieve $v_{\text{in}} = 5 \text{ V}$, the following condition must be verified for the values of R_1 and R_2 :

$$\frac{R_2}{R_1 + R_2} = \frac{5 \text{ V}}{15 \text{ V}}$$

Assuming $\beta = 100$, we can finally obtain:

$$\boxed{R_1 = 30 \Omega, R_2 = 15 \Omega}$$

Exercise 2.6

The minimum current flowing through the R resistor has to be at least equal to the maximum current to the load plus the minimum current to the zener:

$$I_{\text{min},R} = \frac{20 \text{ V} - 10 \text{ V}}{R} \geq 100 \text{ mA} + 10 \text{ mA}$$

Therefore:

$$R \leq \frac{10 \text{ V}}{110 \text{ mA}} = \boxed{91 \Omega}$$

It follows that the maximum power to the zener, selecting $R = 91 \Omega$, is equal to

$$P_{\text{max},z} = \left(\frac{25 \text{ V} - 10 \text{ V}}{91 \Omega} - 0 \text{ A} \right) 10 \text{ V} = \boxed{1.65 \text{ W}}$$

Exercise 2.7

With reference to figure 2.21 of the book, neglecting the current entering the base of the transistor Q , in order to have at least 10 mA flowing through the zener, the resistor R should comply with the following condition:

$$\frac{20 \text{ V} - 10 \text{ V}}{R} \geq 10 \text{ mA}$$

which results in:

$$\boxed{R \leq 1 \text{ k}\Omega}$$

In order to avoid the transistor to be saturated, we want the collector-base voltage to be always higher than zero. This translates in:

$$R_C < R \frac{10 \text{ mA}}{100 \text{ mA}} = 100 \Omega$$

Selecting a conservative value of R_C equal to $\boxed{20 \Omega}$, we can compute the maximum power dissipated by the zener, $P_{\text{max},z}$ and the transistor, $P_{\text{max},Q}$ as:

$$P_{\text{max},z} = \left(\frac{25 \text{ V} - 10 \text{ V}}{1 \text{ k}\Omega} \right) 10 \text{ V} = \boxed{0.15 \text{ W}}$$

$$P_Q = (25 \text{ V} - 20 \Omega I_{\text{load}}) I_{\text{load}}$$

The maximum power dissipated by the transistor is obtained for a collector current equal to 625 mA which is higher than the maximum load current. Therefore, in our case, the maximum power dissipated by Q will be obtained for $I_{\text{load,max}} = 100 \text{ mA}$:

$$P_{\text{max,Q}} = (25 \text{ V} - 20 \Omega I_{\text{load,max}}) I_{\text{load,max}} = \boxed{2.3 \text{ W}}$$

Comparing the results with those of the previous exercise, we notice that the power dissipated by the zener diode significantly decreased but we have an additional power dissipated by the transistor which is higher than the power that the zener diode dissipated in the circuit of the previous exercise. However this power can be decreased by increasing the value of R_C .

Exercise 2.8

In order to keep the emitter voltage V_E in the half range of the dc supply, considering the quiescent current of 5 mA we have:

$$V_E = \frac{15 \text{ V} - (-15 \text{ V})}{2} = 15 \text{ V}$$

and the emitter resistor R_E :

$$R_E = \frac{15 \text{ V}}{5 \text{ mA}} = \boxed{3 \text{ k}\Omega}$$

Since the input impedance to the transistor, under the assumption of a load resistance much larger than the emitter resistance, is:

$$R_{\text{in}} = \beta R_E = 300 \text{ k}\Omega$$

in order to have the 3 dB point below the lowest frequency of 20 Hz, the capacitor C_1 has to be:


$$\frac{1}{R_{\text{in}} C_1} \leq 20 \text{ Hz}$$

meaning that:

$$\boxed{C_1 \geq 0.17 \mu\text{F}}$$

Exercise 2.9

Figure 2.5: Current source circuit

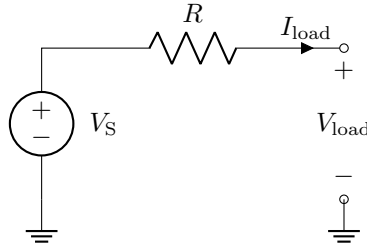

We want:

$$\frac{I_{\text{load}}^{\text{max}} - I_{\text{load}}^{\text{min}}}{I_{\text{load}}^{\text{max}}} = \frac{V_S - 0 \text{ V} - (V_S - 10 \text{ V})}{V_S - 0 \text{ V}} = 0.01$$

from which it follows:

$$\boxed{V_S = 1 \text{ kV}}$$

Exercise 2.10

With reference to Figure 2.5, we assume that I_{load} is equal to 10 mA if V_{load} is equal to 0 V, which means R_{load} is equal to 0Ω . We can therefore calculate R as:

$$R = \frac{V_S}{10 \text{ mA}} = 100 \text{ k}\Omega$$

In this case we have:

$$P_{\text{load}} = 0 \text{ W}, P_R = I_{\text{load}}^2 R = 10 \text{ W}$$

If $V_{\text{load}} = 10 \text{ V}$, from the condition of the previous exercise, we have:


$$I_{\text{load}} = (1 - 0.01)10 \text{ mA} = 9.9 \text{ mA}$$

Therefore:

$$P_{\text{load}} = 10 \text{ V} I_{\text{load}} = 0.1 \text{ W}, P_R = I_{\text{load}}^2 R = 9.8 \text{ W}$$

Exercise 2.11

Figure 2.6: Current sink

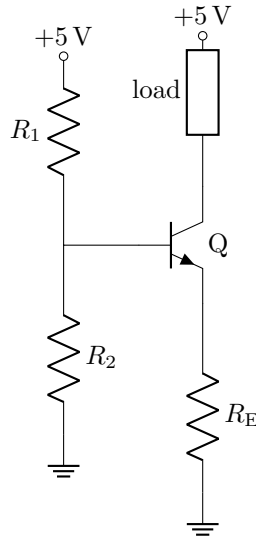

In order to have an emitter current equal to 5 mA, the following condition has to be verified:

$$\frac{R_2}{R_1 + R_2} 5 \text{ V} - 0.6 \text{ V} = R_E 5 \text{ mA}$$

Furthermore, the transistor shouldn't sensibly load the voltage divider, therefore:

$$\frac{R_1 R_2}{R_1 + R_2} \ll R_E \beta$$

Since we have a dc voltage of 5 V, we want the voltage on R_2 to be lower or equal to this value:

$$R_E 5 \text{ mA} + 0.6 \text{ V} \leq 5 \text{ V}$$

leading to:

$$R_E \leq 880 \Omega$$

A good guess value for R_E could be:

$$R_E = 200 \Omega$$

The base voltage will be given by:

$$V_B = R_E 5 \text{ mA} + 0.6 \text{ V} = 1.6 \text{ V}$$

Selecting $R_1 = 1 \text{ k}\Omega$ it is possible to compute R_2 :

$$R_2 = 470 \Omega$$

The impedance seen by the input of the transistor is equal to 320Ω and the input impedance of the transistor, considering $\beta = 100$, is $R_E \beta = 20 \text{ k}\Omega$ with the former much lower than the latter. Finally, considering a maximum V_{CE} voltage of the transistor equal to 0.2 V before it saturates, we obtain the compliance voltage on the load as:

$$V_{\text{comp}} = 5 \text{ V} - (0.2 \text{ V} + R_E 5 \text{ mA}) = 3.8 \text{ V}$$

Exercise 2.12

The distortion is given by:

$$\frac{\Delta V_{\text{out}}}{V_{\text{drop}}} \frac{V_T}{V_T + I_E R_E}$$

therefore, if $R_E = 0 \Omega$ we obtain a predicted distortion equal to $\frac{\Delta G}{G} = \frac{0.2 \text{ V}}{5 \text{ V}} = 0.04$ in case of 0.1 V output

amplitude and $\frac{\Delta G}{G} = \frac{2 \text{ V}}{5 \text{ V}} = 0.4$ in case of 1 V output amplitude. If $R_E I_E = 0.25 \text{ V}$, $\frac{\Delta G}{G}$ equals to 0.004 and 0.04 for output voltage amplitudes equal to 0.1 V and 1 V , respectively.

Exercise 2.13

If the transistor is biased at half V_{cc} , we have that the collector-emitter voltage will be equal to $V_{CE} = V_{cc} - I_C R_C = V_{cc} - V_{cc}/2 = V_{cc}/2$ where I_C is the collector quiescent current and R_C is the collector resistor. The collector-base voltage will be therefore $V_{CB} = V_{cc}/2 - V_{BE}$. In this case V_{BE} is supposed to be obtained by means of a voltage divider. If the temperature changes, approximately V_{BE} does not change and the collector current will increase by $9\% \text{ } ^\circ\text{C}^{-1}$. This means that the collector current doubles for a temperature increase equal to 8°C . In this case $R_C I_C$ becomes equal to $2V_{cc}/2 = V_{cc}$. As a consequence

$$V_{CB} = -V_{BE} < 0 \text{ and the transistor goes in saturation.}$$

Exercise 2.14

The bias is arranged in order to have a collector current equal to 1 mA . Indeed:

$$I_c = \frac{0.775 \text{ V} - 0.6 \text{ V}}{175 \Omega} = 1 \text{ mA}$$

The base-emitter voltage decreases by $2.1 \text{ mV } ^\circ\text{C}^{-1}$. Therefore, if the temperature increases by 20°C , the collector current will become:

$$I_c = \frac{0.775 \text{ V} - 0.6 \text{ V} - 0.0021 \text{ V } ^\circ\text{C}^{-1} 20^\circ\text{C}}{175 \Omega} = 0.76 \text{ mA}$$

It can be seen that the new collector current is about 25% lower than 1 mA

Exercise 2.15

The voltage gain is given by:

$$G = \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{R_C}{r_e} = \frac{I_C R_C}{V_T}$$

In order to achieve a voltage drop on R_C equal to half the V_{cc} voltage:

$$I_C R_C = \frac{1}{2} V_{cc}$$

and therefore:


$$R_C = \frac{1}{2} \frac{V_{cc}}{I_C}$$

Substituting the R_C expression into the voltage gain:

$$G = \frac{1}{2} \frac{V_{cc}}{V_T} = \frac{V_{cc}}{50 \text{ mV}} = 20 V_{cc}$$

Exercise 2.16

Figure 2.7: Tuned common emitter amplifier

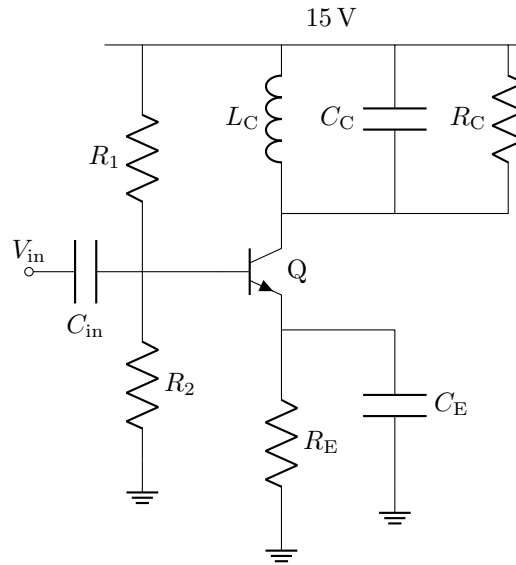

With reference to Figure 2.7, we start by choosing the emitter resistor R_E . We want its value to be large enough to have a voltage drop higher than V_{BE} in order to have a good stability of the quiescent current with the temperature. However we want the transistor to operate in the active region. Since at DC, the inductor behaves like a short circuit, we have that the collector voltage is equal to V_{cc} , therefore:

$$R_E I_E^Q < V_{cc} - 0.2 \text{ V}$$

and

$$R_E < \frac{V_{cc} - 0.2 \text{ V}}{I_E^Q} = 14.8 \text{ k}\Omega$$

where I_E^Q is equal to about 1 mA. We choose:

$$R_E = 1 \text{ k}\Omega$$

In order to achieve a quiescent current equal to 1 mA, the base voltage has to be equal to:

$$V_B = 0.6 \text{ V} + R_E I_E^Q = 1.6 \text{ V}$$

Therefore, the ratio between R_1 and R_2 has to be equal to 8.4. Choosing the parallel resistance of R_1 and R_2 to be about one tenth of the transistor input resistance $\beta R_E \approx 100 \text{ k}\Omega$ we choose the following values for R_1 and R_2 :

$$R_1 = 84 \text{ k}\Omega, \quad R_2 = 10 \text{ k}\Omega$$

The value of the capacitor C_C can be obtained forcing the parallel LC circuit to resonate at 100 kHz:

$$\frac{1}{2\pi} \sqrt{\frac{1}{L_C C_C}} = 100 \text{ kHz}$$

Therefore:

$$C_C = 2.5 \text{ nF}$$

The value of the capacitor C_E can be selected imposing that the absolute value of the impedance of the parallel between R_E and C_E is lower than $r_e = 25 \Omega$ for a quiescent current of 1 mA. Doing the math we obtain:

$$C_E > \frac{\sqrt{\frac{R_E^2}{25 \Omega} - 1}}{\omega R_E} = 63.6 \text{ nF}$$

A value of C_E equal to 10 μF is conservative enough to maximise the AC gain:

$$C_E = 10 \mu\text{F}$$

It remains to calculate the value of the input decoupling capacitor C_{in} . Its value can be obtained by forcing the cut-off frequency $1/R_{in}$ to be below 100 kHz where

$$R_{eq} = \beta r_e || R_1 || R_2$$

where we neglected the emitter impedance which is verly low thanks to the C_E effect. We have therefore:

$$C_{in} \geq 5 \text{ nF}$$

Even in this case a conservative value for C_{in} can be:

$$C_{in} = 10 \mu\text{F}$$

Exercise 2.17

In the following, the pedix B, C and E refer to base, collector and emitter. The apix Q1, Q2 and Q3 refer to the relevant transistors. Supposing all the transistors share the same β , the I_P current can be expressed as:

$$I_P = I_C^{Q1} + I_B^{Q3} = \beta I_B^{Q1} + \frac{I_C^{Q3}}{\beta}$$

Since the base-emitter voltage of the transistor Q1 is the same of the transistor Q2, the base currents are the same. Therefore:

$$I_B^{Q1} + I_B^{Q2} = 2I_B^{Q1} = I_E^{Q3} - I_C^{Q1} = \frac{\beta + 1}{\beta} I_C^{Q3} - \beta I_B^{Q1}$$

and then:

$$I_B^{Q1} = \frac{\beta + 1}{\beta(\beta + 2)} I_C^{Q3}$$

Substituting this expression into the first equation, it is possible to obtain the following expression for I_P :

$$I_P = \left(1 + \frac{2}{\beta(\beta + 2)}\right) I_C^{Q3} \approx I_C^{Q3}$$

By comparing the above expression with that that typical of a basic current mirror:

$$I_P = \left(1 + \frac{2}{\beta}\right) I_C$$

one can see that the load current I_C^{Q3} is much closer to the reference current I_P than for the basic current mirror. Indeed:

$$\frac{2}{\beta(\beta + 2)} \ll \frac{2}{\beta}$$

Exercise 2.18

For a grounded differential amplifier, the differential gain is:

$$G_{\text{diff}} = \frac{R_C}{2r_e} = \frac{R_C I_C}{2V_T} = V_C 2V_{\text{ext}} T = \boxed{20V_C}$$

where V_C is the voltage drop across the collector resistor R_C . Therefore, if $V_C = 0.5V_{\text{cc}}$:


$$\boxed{G_{\text{diff}} = 10V_{\text{cc}}}$$

Following a similar argument:

$$\text{CMRR} = \frac{R_1}{r_e} = \frac{R_1 I_C}{V_T} = \frac{1}{2} V_1 V_T = \boxed{20V_1}$$

where V_1 is the voltage drop across the R_1 resistor.

Figure 2.8: Tuned common emitter amplifier

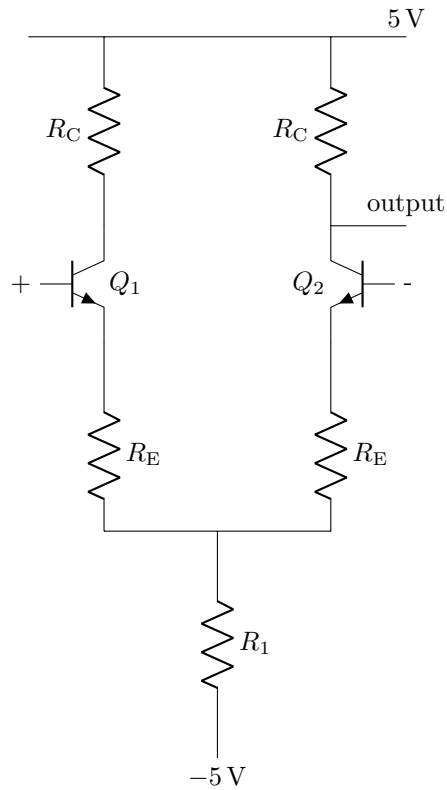

For the differential, single-ended amplifier in Figure 2.8, the output impedance is equal to R_C . Therefore we have $R_C = 10 \text{ k}\Omega$. Since we want the voltage drop on the collector resistor to be half of the V_{cc} :

$$I_C = 2.5 \text{ V} / 10 \text{ k}\Omega = 250 \text{ }\mu\text{A}$$

Neglecting the voltage drop on the emitter resistor R_E , we can approximate the collector current as:

$$I_C \approx \frac{5 \text{ V} - 0.6 \text{ V}}{2R_1}$$

and therefore:

$$R_1 = 2.8 \text{ k}\Omega$$

The value of R_E can then be obtained from the differential gain, considering that it is given by:

$$G_{\text{diff}} = 25 = \frac{R_C}{2(r_e + R_E)}$$


. Therefore, considering that $r_e = V_T / I_C = 100 \Omega$:

$$R_E = 100 \Omega$$

Exercise 2.19

As regards the differential amplifier in Figure 2.84 of the book, the AC voltage across the C_{CB} capacitor is equal to the voltage at the base of the transistor Q_1 without depending on the voltage gain. The voltage across the emitter resistor R_E is the input to a common base amplifier which does not have Miller effect.

Figure 2.9: Cascode amplifier

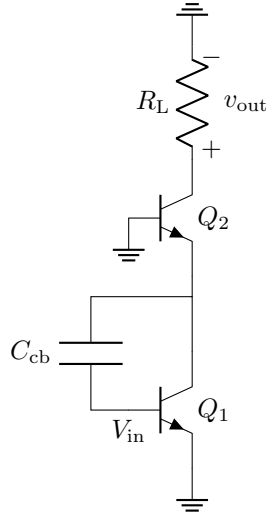

As regards the cascode configuration, one can make reference to Figure 2.9. Under the approximation that the collector current of the transistor Q_1 is equal to that of the transistor Q_2 :

$$i_C^{Q_1} = i_C^{Q_2} = \frac{v_{in}}{r_e^{Q_1}}$$

where $r_e^{Q_1}$ is the differential resistance of the Q_1 transistor. The output voltage will be:

$$v_{out} = R_L i_C^{Q_2}$$

The base-emitter AC voltage of the Q_2 transistor will be:

$$v_{BE}^{Q_2} = r_e^{Q_2} i_C^{Q_2}$$

where $r_e^{Q_2}$ is the differential resistance of the Q_2 transistor.

The voltage across the C_{CB} capacitor will be:

$$v_{CB} = v_{in} + v_{BE}^{Q_2} = v_{in} + \frac{v_{in} r_e^{Q_2}}{r_e^{Q_1}}$$

It follows that the amplitude of the current through the C_{CB} capacitor is:

$$I_{CB} = \frac{v_{in} \left(1 + \frac{r_e^{Q_2}}{r_e^{Q_1}} \right)}{X_{CB}}$$

where X_{CB} is the capacitive reactance associated to the C_{CB} capacitor. The Miller capacitance C_{CB}^M is therefore:

$$C_{CB}^M = C_{CB} \left(1 + \frac{r_e^{Q_2}}{r_e^{Q_1}} \right)$$

and does not depend on the voltage gain of the cascode amplifier.

Exercise 2.20

The expression for the input impedance of the inverting amplifier is straightforward by considering that it is the series between the R_1 resistance with the input impedance of the transresistance amplifier. Therefore, the input impedance Z_{in} is:

$$Z_{in} = R_1 + R_{in} \parallel \frac{R_2}{1 + A}$$

The closed loop gain can also be obtained in a straightforward way starting by considering the input impedance of the operational amplifier, R_{in} , approaching to infinity. In this case, all the current flowing in R_1 goes in R_2 making R_1 and R_2 in series. Therefore:

$$V_{out} = vA$$

where v is the differential voltage of the operational amplifier and A is the open loop gain. v is given by:

$$v = -[V_{in} - (V_{in} - V_{out})B]$$

where B is defined as:

$$\frac{R_1}{R_1 + R_2}$$

The expression for the output voltage becomes:

$$V_{out} = -A[V_{in} - (V_{in} - V_{out})B]$$

and the closed loop gain is:


$$G = \frac{V_{out}}{V_{in}} = -A \frac{1 - B}{1 + AB}$$

Exercise 2.21

$$G_{CL} = \frac{-100j}{1 + -100j(0.1)} = 9.90 - 0.99j$$

Exercise 2.22

Figure 2.10: Open loop small signal circuit

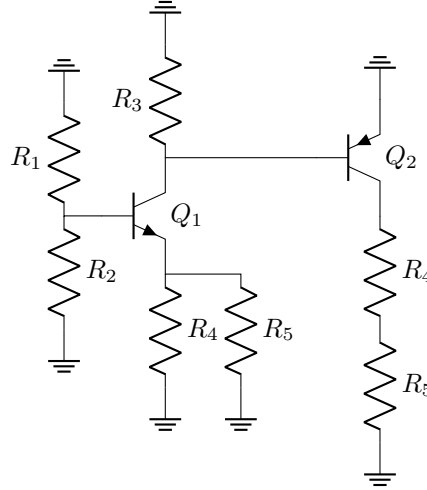

The feedback takes the voltage from the output of Q2 transistor and returns it to the input of the Q1 transistor through a voltage divider made of the resistors R_4 and R_5 . The feedback is of *voltage-voltage* kind. In order to account of the feedback loading effect in opening the loop, the reference circuit is that of Figure 2.10. Considering a β of 100 for both Q1 and Q2, the open loop gain is:

$$G^{\text{OL}} = \frac{-1}{r_e^{\text{Q1}} + R_4 \parallel R_5} [R_3 \parallel r_e^{\text{Q2}} \beta] \left[-\frac{R_4 + R_5}{r_e^{\text{Q2}}} \right] \approx \frac{1}{r_e^{\text{Q1}} + R_4} [R_3 \parallel r_e^{\text{Q2}} \beta] \left[\frac{R_5}{r_e^{\text{Q2}}} \right]$$

Therefore, since $r_e^{\text{Q1}} = r_e^{\text{Q2}} = 25 \Omega$:

$$G^{\text{OL}} \approx 200$$

The feedback gain is:

$$B = \frac{R_4}{R_4 + R_5} \approx \frac{R_4}{R_5} = 0.1$$

Therefore, the loop gain is:

$$G^{\text{OL}} B \approx 20$$

The open loop output impedance is:

$$Z_{\text{out}}^{\text{OL}} = R_4 + R_5 \approx R_5 = 10 \text{ k}\Omega$$


The closed loop parameters are therefore:

$$G^{\text{CL}} = \frac{G^{\text{OL}}}{1 + G^{\text{OL}} B} \approx 9.5$$

$$Z_{\text{out}}^{\text{CL}} = \frac{Z_{\text{out}}^{\text{OL}}}{1 + G^{\text{OL}} B} \approx \frac{Z_{\text{out}}^{\text{OL}}}{G^{\text{OL}} B} = 500$$

Exercise 2.23

Figure 2.11: Solution

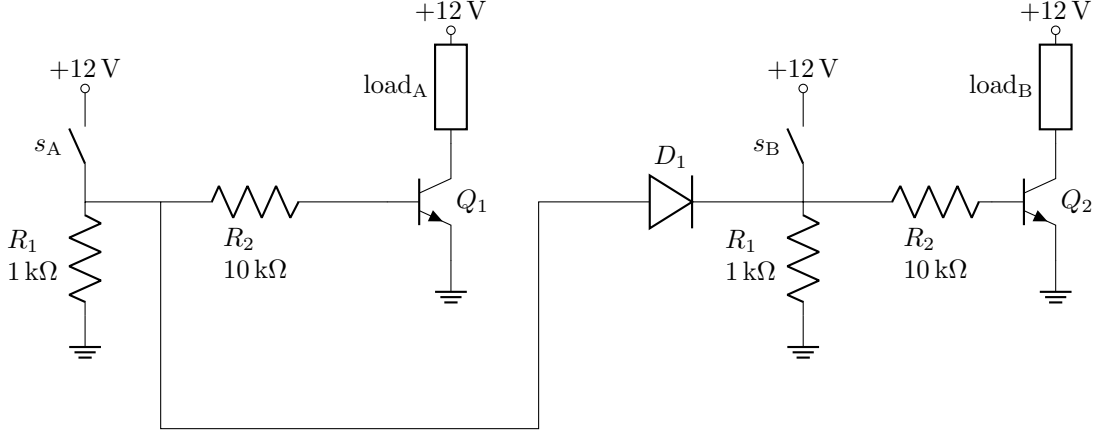

Let's suppose the loads are resistive with a resistance equal to 150Ω and both the npn transistors have $\beta = 100$. When s_A and s_B are open, both Q_1 and Q_2 bases are to ground and no current flows into the loads.

If s_A is closed, the left terminals of the R_2 resistors are at 12 V (minus a diode voltage drop for the resistor connected at the Q_2 base). The base currents are therefore:

$$I_b = \frac{12\text{ V} - 0.6\text{ V}}{10\text{ k}\Omega} = 1.14\text{ mA}$$

Such a base current, with the considered β and load resistance, causes Q_1 and Q_2 to saturate. Therefore, the load current is:

$$I_1^A = I_1^B = \frac{12\text{ V} - 0.2\text{ V}}{150\Omega} = 79\text{ mA}$$

When s_A is open and s_B is closed, D_1 is reverse biased and Q_1 is in cutoff region since no current flows into its base. However, 1.14 mA flows into the base of Q_2 which goes into saturation.

Exercise 2.24

(a) Under the assumption that β is very large, the load current I_{load} is given by:

$$I_{\text{load}} = I_C \approx I_E \left[\frac{V_{CC}R_2}{R_1 + R_2} - 0.6\text{ V} \right] \frac{1}{R_E}$$

where $V_{CC} = 10\text{ V}$, $R_1 = 8.2\text{ k}\Omega$, $R_1 = 1.6\text{ k}\Omega$ and $R_1 = 1.5\text{ k}\Omega$. Therefore $I_{\text{load}} = 0.7\text{ mA}$ Since for the transistor to work in active region it must hold:

$$V_{CE} = V_{CC} - V_{\text{load}} - V_E \geq 0.2\text{ V}$$

since $V_E = I_E R_E \approx 1\text{ V}$ the output compliance is given by:

$$V_{\text{load}} \leq 8.8\text{ V}$$

- (b) Removing the assumption that β is very large, has two effects. First, the emitter current and the collector currents are no more equal:

$$I_{\text{load}} = I_C = \beta \frac{1}{\beta + 1} I_E$$

Second, the R_1 and R_2 resistors are no more in series since the base current is no more negligible. The full expression for the emitter current can be obtained by considering that:

$$\begin{aligned} I_E &= I_B + I_C \\ I_1 &= I_B + I_2 \end{aligned}$$

where I_1 and I_2 are the currents flowing through R_1 and R_2 , respectively, and I_B is the base current. Under this conditions, the emitter current is given by:

$$I_E = \frac{1}{R_E} \left[\frac{V_{CC} R_2}{R_1 + R_2} - 0.6 \text{ V} \right] \left[1 + \frac{R_2}{R_1(\beta + 1)} \left(1 - \frac{R_2}{R_1 + R_2} \right) \right]^{-1}$$

It follows:

$$\begin{aligned} \beta = 50 \quad I_E &= 0.685 \text{ mA} \quad I_{\text{load}} = I_C = 0.67 \text{ mA} \\ \beta = 100 \quad I_E &= 0.688 \text{ mA} \quad I_{\text{load}} = I_C = 0.68 \text{ mA} \end{aligned}$$

- (c) Here we consider again that β is very large. Being R_1 and R_2 in series, the base voltage does not change due to early effect and we can write:

$$\Delta I_E = -\frac{\Delta V_{BE}}{R_E} = \frac{0.0001 \Delta V_{CE}}{R_E}$$

Furthermore:

$$\Delta V_{CE} = -\Delta V_{\text{load}} - \Delta I_E R_E$$

Solving for ΔI_E :

$$\Delta I_{\text{load}} = \Delta I_C \approx \Delta I_E = \frac{-0.0001}{1.0001 R_E} \Delta V_{\text{load}}$$

For an output voltage within the output compliance ($\Delta V_{\text{load}} = 8.8 \text{ V}$):

$$\boxed{\Delta I_{\text{load}} = -66.7 \text{ nA}}$$

- (d) V_{BE} varies by $-2.1 \text{ mV } ^\circ\text{C}^{-1}$. With respect to the load current computed at the first point (a) ($I_{\text{load}} = 0.7 \text{ mA}$) it is easy to see that:


$$\boxed{\frac{\Delta I_{\text{load}}}{\Delta ^\circ\text{C}} = 0.2 \% ^\circ\text{C}^{-1}}$$

In order to account for the variation of β with temperature, we have to use the expression obtained in point b. In this case we obtain:

$$\boxed{\frac{\Delta I_{\text{load}}}{\Delta ^\circ\text{C}} = 0.21 \% ^\circ\text{C}^{-1}}$$

Exercise 2.25

Figure 2.12: Common emitter amplifier

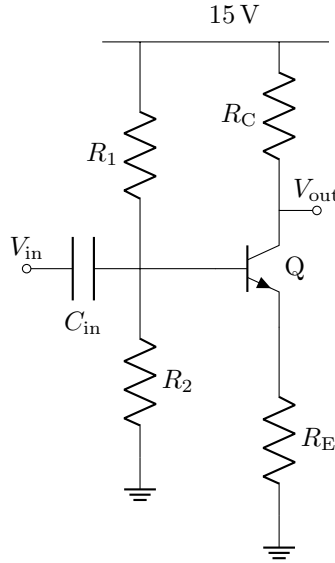

The gain is approximately given by:

$$G = \frac{R_C}{R_E} = 15$$

Given a bias collector current of 0.5 mA, in order to have the bias collector voltage at $0.5V_{CC} = 7.5\text{ V}$, the collector resistance has to be equal to:

$$R_C = \frac{7.5\text{ V}}{0.5\text{ mA}} = 15\text{ k}\Omega$$

It follows that $R_E = 1\text{ k}\Omega$ In order to have a bias collector current equal to 0.5 mA, the following condition must hold:

$$I_C \approx I_E = \frac{V_B - 0.6\text{ V}}{R_E}$$

meaning that $V_B = 1.1\text{ V}$ This defines the first out of three conditions on the value of the resistors R_1 and R_2 :

$$V_{CC} \frac{R_2}{R_1 + R_2} = 1.1\text{ V} \rightarrow R_1 = 12.64 R_2$$

The second condition can be obtained by considering the maximum emitter voltage:

$$V_E^{\text{MAX}} = R_E I_E^{\text{MAX}} = 1\text{ k}\Omega 1\text{ mA} = 1\text{ V}$$

the minimum current flowig through R_1 is:

$$I_{R_1}^{\text{MIN}} = \frac{V_{CC} - 1.6\text{ V}}{R_1} = \frac{13.4\text{ V}}{R_1}$$

In order to properly drive the base of the transistor, this current has to be higher than the maximum base current:

$$\frac{13.4 \text{ V}}{R_1} > \frac{1 \text{ mA}}{\beta}$$

leading to the second condition:

$$R_1 < 1.34 \text{ M}\Omega$$

Finally, the input impedance of the transistor should be much higher than the parallel impedance of R_1 and R_2 :

$$\frac{R_1 R_2}{R_1 + R_2} \ll \beta R_E = 100 \text{ k}\Omega$$

Taking into account these conditions, we select the following values for R_1 and R_2 :

$$R_1 = 20.2 \text{ k}\Omega, R_2 = 1.6 \text{ k}\Omega$$

To be sure the 3 dB point is below the frequency of interest (100 Hz), the value of the input capacitor can be computed by:


$$\frac{1}{1.5 \text{ k}\Omega C_{\text{in}}} < 2\pi 100 \text{ Hz}$$

where $1.5 \text{ k}\Omega$ is the value of the parallel R_1 and R_2 . From the previous expression one can obtain the value of the input capacitance C_{in} :

$$C_{\text{in}} > 1.06 \text{ }\mu\text{F}$$

Exercise 2.26

Figure 2.13: Bootstrapped common emitter amplifier

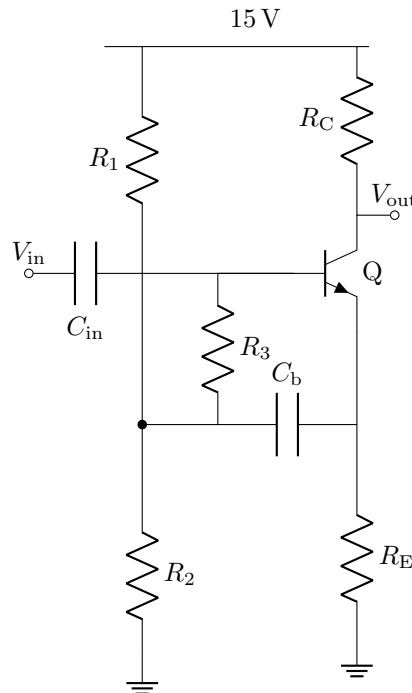

From a small signal perspective, the equivalent R_3 resistance is given by:

$$R_{eq} = \frac{R_3}{1 - A}$$

where A is the voltage gain of the emitter follower and it is given by:

$$\frac{R_E g_m}{1 + R_E g_m} = 0.95$$

since $g_m = \frac{0.5 \text{ mA}}{25 \text{ mV}} = 0.02 \text{ S}$ Therefore $R_{eq} \approx 20R_3$.


We can choose $R_3 = 4.7 \text{ k}\Omega$ to obtain a $R_{eq} = 94 \text{ k}\Omega$ The resistance seen by the C_b capacitor is equal to:

$$R_1 || R_2 || (R_{eq} + 100 \text{ k}\Omega) \approx 1.5 \text{ k}\Omega$$

Therefore we want the capacitive impedance of C_b at 100 Hz to be much lower than 1.5 k Ω . Choosing a $C_b = 10 \text{ }\mu\text{F}$ should be enough.

Exercise 2.27

Figure 2.14: Differential pair and emitter follower

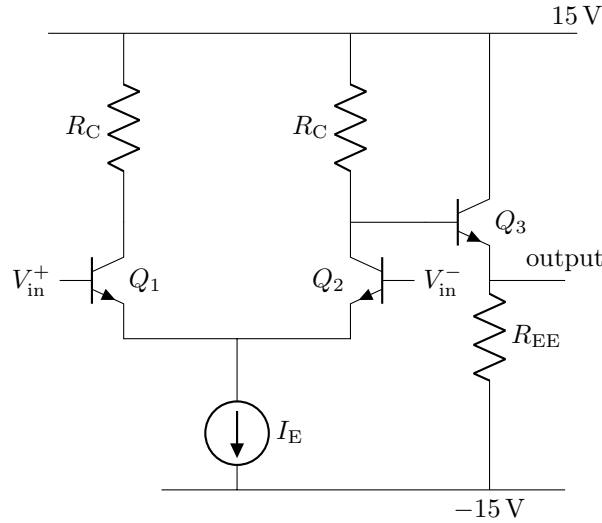

At DC, when $V_{in}^+ = V_{in}^- = 0 \text{ V}$ the current I_E is splitted equally between Q_1 and Q_2 . Therefore, if the emitter current of both transistors has to be equal to 0.1 mA we have that $I_E = 0.2 \text{ mA}$ The differential gain G_d has to be equal to 50:

$$G_d = \frac{R_C}{2r_E} = 50$$


Since $R_E = 25 \text{ mV}/0.1 \text{ mA} = 250 \text{ }\Omega$, we have that $R_C = 25 \text{ k}\Omega$ If we also want the bias current of transistor Q_3 to be equal to 0.1 mA:

$$R_{EE} = \frac{15 \text{ V} + 15 \text{ V} - 0.6 \text{ V} - R_C 0.1 \text{ mA}}{0.1 \text{ mA}} \approx 270 \text{ k}\Omega$$

As a final note, the differential pair is not degenerated. This led to a lower resistance R_C but to a higher resistance R_{EE} and a very small linearity region.

Exercise 2.28

Figure 2.15: Differential pair with current source emitter

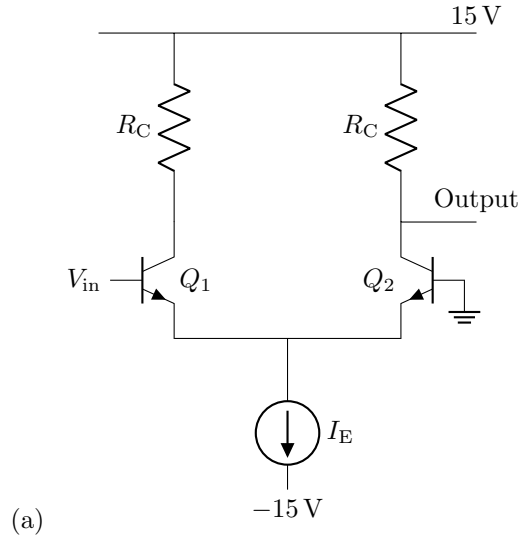


The quiescent current I_E will be equally divided among the two transistors Q_1 and Q_2 . Therefore, in order to have a collector current equal to $100\ \mu\text{A}$, $I_E = 200\ \mu\text{A}$. The gain of the single ended input-output differential pair can be easily computed by considering that the equivalent resistance as seen from Q_2 emitter is equal to $r_E^{Q_2}$. Therefore, the gain will be equal to:

$$G = \frac{R_C}{r_E^{Q_1} + r_E^{Q_2}} = \frac{R_C}{2r_E} = 20$$

since:

$$r_E^{Q_1} = r_E^{Q_2} = r_E = \frac{25\ \text{mV}}{100\ \mu\text{A}} = 250\ \Omega$$

Figure 2.16: Differential pair with variable current emitter

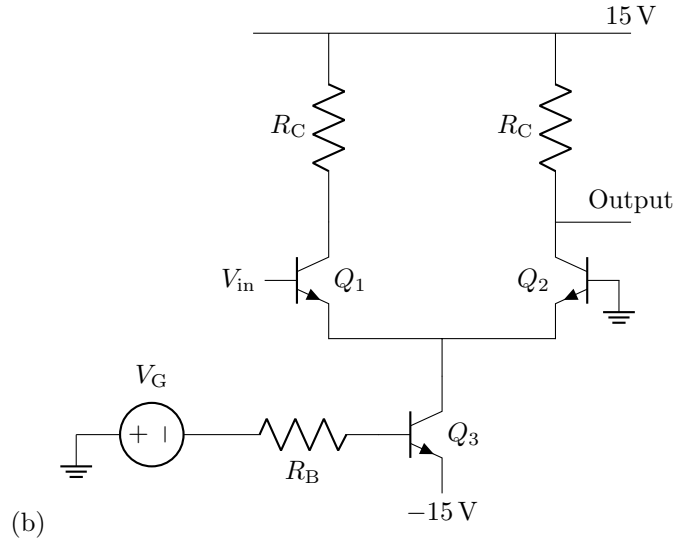

In the circuit of Figure 2.16, the DC voltage V_G tunes the base current into the transistor Q_3 changing the quiescent current into the transistors Q_1 and Q_2 . The value of the resistor R_B can be obtained by imposing that the maximum V_G voltage that doesn't saturate the transistors Q_1 and Q_2 is 10 V. By virtue of the V_{BE} of Q_2 , the emitter of Q_1 and Q_2 is at -0.6 V with respect to ground. Therefore, the maximum collector current that doesn't cause Q_1 and Q_2 to saturate can be obtained as:

$$I_C^{\max} = \frac{15 \text{ V} + 0.6 \text{ V} - 0.2 \text{ V}}{R_C} = 1.54 \text{ mA}$$

The Q_3 maximum collector current will be twice I_C^{\max} . Therefore, we have:

$$\beta \frac{15 \text{ V} - 10 \text{ V} - 0.6 \text{ V}}{R_B} = 2I_C^{\max}$$

which gives:

$$\boxed{R_B = 143 \text{ k}\Omega}$$

In order to compute the gain, first we have to compute the value of the quiescent collector current of Q_1 and Q_2 . This will be equal to:

$$I_C^Q = \beta \frac{1}{2} \frac{15 \text{ V} - 0.6 \text{ V} - V_G}{R_B}$$

The gain will be equal to:

$$\boxed{G = \frac{1}{2} \frac{I_C^Q R_C}{25 \text{ mV}} \approx 70 (14.4 \text{ V} - V_G)}$$

Exercise 2.29

(a) Since the quiescent point is equal to $0.5V_{CC}$, the quiescent collector current can be computed as:

$$I_C = \frac{1}{2} \frac{20 \text{ V}}{10 \text{ k}\Omega} = 1 \text{ mA}$$

Using the Ebers-Moll equation to derive the base quiescent voltage:

$$V_{BE} = V_T \ln \left(\frac{I_C}{I_S} \right) = 0.69 \text{ V}$$

with a saturation current I_S equal to $1 \times 10^{-15} \text{ A}$, it is possible to estimate the value of the variable resistor R that leads to this voltage:

$$R = \frac{1 \text{ k}\Omega \cdot 0.69 \text{ V}}{20 \text{ V} - 0.69 \text{ V}} = 35.8 \Omega$$

The input impedance will be therefore the parralle between $1 \text{ k}\Omega$, 35.8Ω and βr_E , being r_E the differential resistance of the transistor:

$$r_E = \frac{I_C}{V_T} \approx 25 \Omega$$

It follows that the input impedance Z_{in} is approximately equal to 34Ω

- (b) The differential gain is equal to the ratio between the collector resistor and the differential resistor R_E . Therefore:

$$G = \frac{10 \text{ k}\Omega}{25 \Omega}$$

- (c) Since the collector quiescent current approximately changes by $9\% \text{ } ^\circ\text{C}^{-1}$, it is easily seen that its amount doubles for a temepreature change of $8 \text{ } ^\circ\text{C}$. This leads to a quiescent collector voltage equal to 20 V causing the transistor to saturate.

Exercise 2.30

The bias base current into Q_1 ($I_B^{Q_1}$) is the sum of the input bias current (from *input 1*: I^{I1}) and the collector current from the Q_4 transistor of the current mirror made of Q_4 and Q_3 ($I_C^{Q_4}$):

$$I_B^{Q_1} = I^{I1} + I_C^{Q_4}$$

Therefore:

$$I^{I1} = I_B^{Q_1} - I_C^{Q_4}$$

Since Q_1 and Q_2 are beta matched, their base currents are the same since sharing the same collector current. The current mirror copies the base current of Q_2 on Q_4 and therefore $I_C^{Q_4} = I_B^{Q_1}$. It follows that:

$$I^{I1} = I_B^{Q_1} - I_C^{Q_4} = 0 \text{ A}$$

In order for the circuit to operate correctly, all transistors have to work in active operation region. For this to be verified, the collector-base voltage has to be higher than zero for all transistors. Here the collector-base voltage of the transistor Q_1 is the critical one.

$$V_{CB}^{Q_1} = -0.6 \text{ V} - V_{CB}^{Q_4}$$

$$V_{CE}^{Q_4} = V_E + 0.6 \text{ V} - V_M$$

where V_M is the bias voltage applied to the emitters of the current mirror.

$$V_{CB}^{Q_4} = V_{CE}^{Q_4} + 0.6 \text{ V} = V_E + 1.2 \text{ V} - V_M$$

By replacing the expression for $V_{\text{CB}}^{Q_4}$ into that of $V_{\text{CB}}^{Q_1}$ one finds:

$$V_{\text{CB}}^{Q_1} = V_{\text{M}} - V_{\text{E}} - 1.8 \text{ V}$$

If we want this to be higher than zero:

$$V_{\text{M}} > V_{\text{E}} + 1.8 \text{ V}$$

$V_{\text{M}} = V_{\text{E}} + 2 \text{ V}$ is a quite safe value
